

# Parallel Data Processing in Reconfigurable Systems

## Lecture 1

2014/2015

Introduction to Nexys-4 prototyping board  
and Vivado Design Suite

Iouliia Skliarova




Universidade  
de Aveiro

# Contents

- Brief overview of Nexys-4 prototyping board
- Introduction to Vivado Design Suite
  - understand the design flow
  - create and debug VHDL designs
  - configure the FPGA
- Development of test benches in VHDL and simulation in Vivado
  - perform simulation verification
- Specification of embedded and distributed memories
  - describe memories in VHDL
  - create and integrate IP cores into design flow using IP Catalog
  - initialize memories from files
- Useful modules for lab 1
  - clock divider
  - debouncer
  - 7-segment display control


# Nexys-4 board

 

- Manufactured by Digilent
- Contains an FPGA of Artix-7 family
- Configured directly from Vivado through USB JTAG/UART


Picture from Nexys4™ FPGA Board Reference Manual

# Nexys-4 components

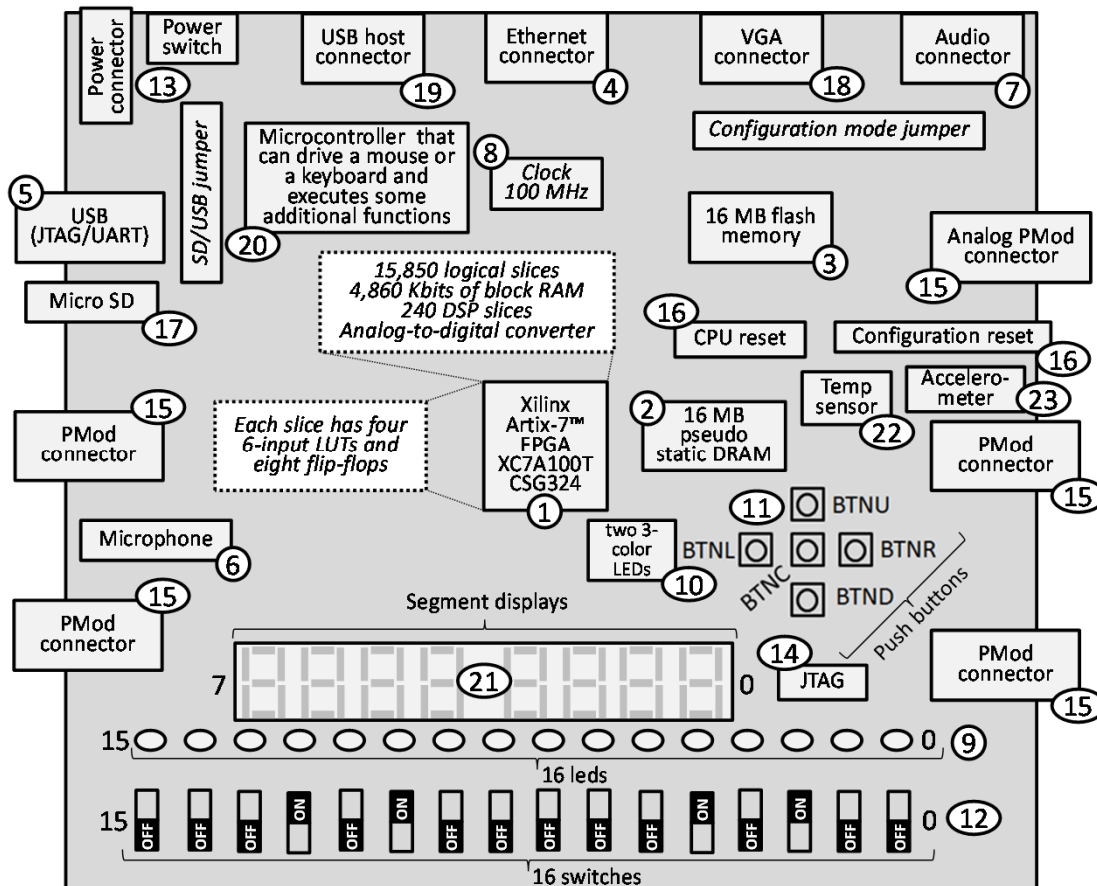

1. Xilinx Artix-7™ FPGA xc7a100t-1csg324
2. 128Mb=16MB cellular RAM
3. 128 Mb=16MB SPI (quad-SPI) Flash
4. 10/100 Ethernet
5. USB-JTAG programming and USB-UART
6. Microphone
7. Audio connector
8. 100 MHz clock oscillator
9. 16 user LEDs
10. Two 3-color user LEDs
11. 5 user buttons
12. 16 slide switches
13. Power connector and power-on LED indicator
14. JTAG port
15. Pmod expansion connectors (2×6)
16. Two reset buttons
17. Micro SD card slot
18. VGA connector
19. USB host connector
20. Microcontroller
21. Eight 7-segment displays
22. Temperature sensor
23. Accelerometer

# Basic I/O

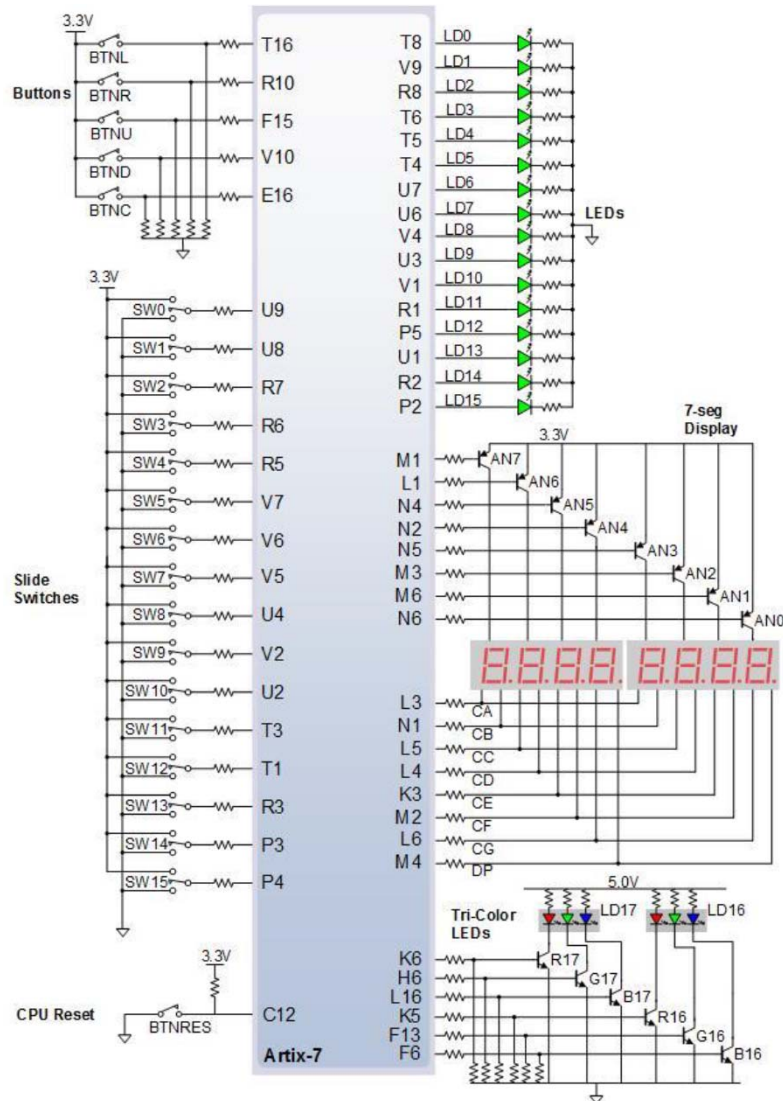

Picture from Nexys4™ FPGA Board Reference Manual

- The five **pushbuttons** generate a low output when they are at rest, and a **high output** only **when** they are **pressed**.
- **Slide switches** generate constant high or low inputs depending on their position.
- The sixteen individual **LEDs** are anode-connected to the FPGA via resistors, so they will **turn** on when a logic **high voltage** is applied to their respective I/O pin.
- The anodes of the seven LEDs forming each 7-segment display digit are tied together into one “common anode” circuit node, but the LED cathodes remain separate. The common anode signals are available as eight “digit enable” input signals to the 8-digit display. The cathodes of similar segments on all the displays are connected into seven circuit nodes. This signal connection scheme creates a multiplexed display, where the cathode signals are common to all digits but they can only illuminate the segments of the digit whose corresponding anode signal is asserted. To illuminate a segment, both the **anode** and the **cathode** should be driven **low**.


# Xilinx Artix-7™ FPGA xc7a100t-1csg324

- Xilinx® 7 series FPGAs include three families:
  - The Artix®-7 family is optimized for lowest cost and power for the highest volume applications.
  - The Virtex®-7 family is optimized for highest system performance and capacity.
  - The Kintex®-7 family is an innovative class of FPGAs optimized for the best price-performance.
- Artix-7 xc7a100t feature summary:
  - 15,850 logic slices, each with four 6-input LUTs and 8 flip-flops
  - 4,860 Kbits of fast block RAM (135 × 36 Kb blocks)
  - 6 clock management tiles, each with phase-locked loop (PLL)
  - 240 DSP slices (with 25 × 18 multiplier, 48-bit accumulator, and pre-adder)
  - On-chip analog-to-digital converter (XADC)
  - Configuration bitstream length of 30,606,304 bits (~3.6 MB)
- Nexys-3 FPGA (Xilinx Spartan®-6 XC6LX16-CS324):
  - 2,278 logic slices, each with four 6-input LUTs and 8 flip-flops
  - 576 Kbits of fast block RAM (32 × 18 Kb blocks)
  - 2 clock management tiles, each with phase-locked loop (PLL)
  - 32 DSP slices (with 18 × 18 multiplier, 48-bit accumulator, and pre-adder)
  - Configuration bitstream length of 3,731,264 bits (~3.6 Mb)



# Vivado IDE solution

- 7-Series (or newer) devices
- Interactive design and analysis
  - Timing analysis, connectivity, resource utilization, timing constraint analysis and I/O assignment
- RTL development and analysis
  - Elaboration of HDL
  - Hierarchical exploration
  - Schematic generation
- XSIM simulator integration
- Full Tcl scripting support
- Interactive IP plug & play environment
- Synthesis and implementation in one package

# FPGA design flow

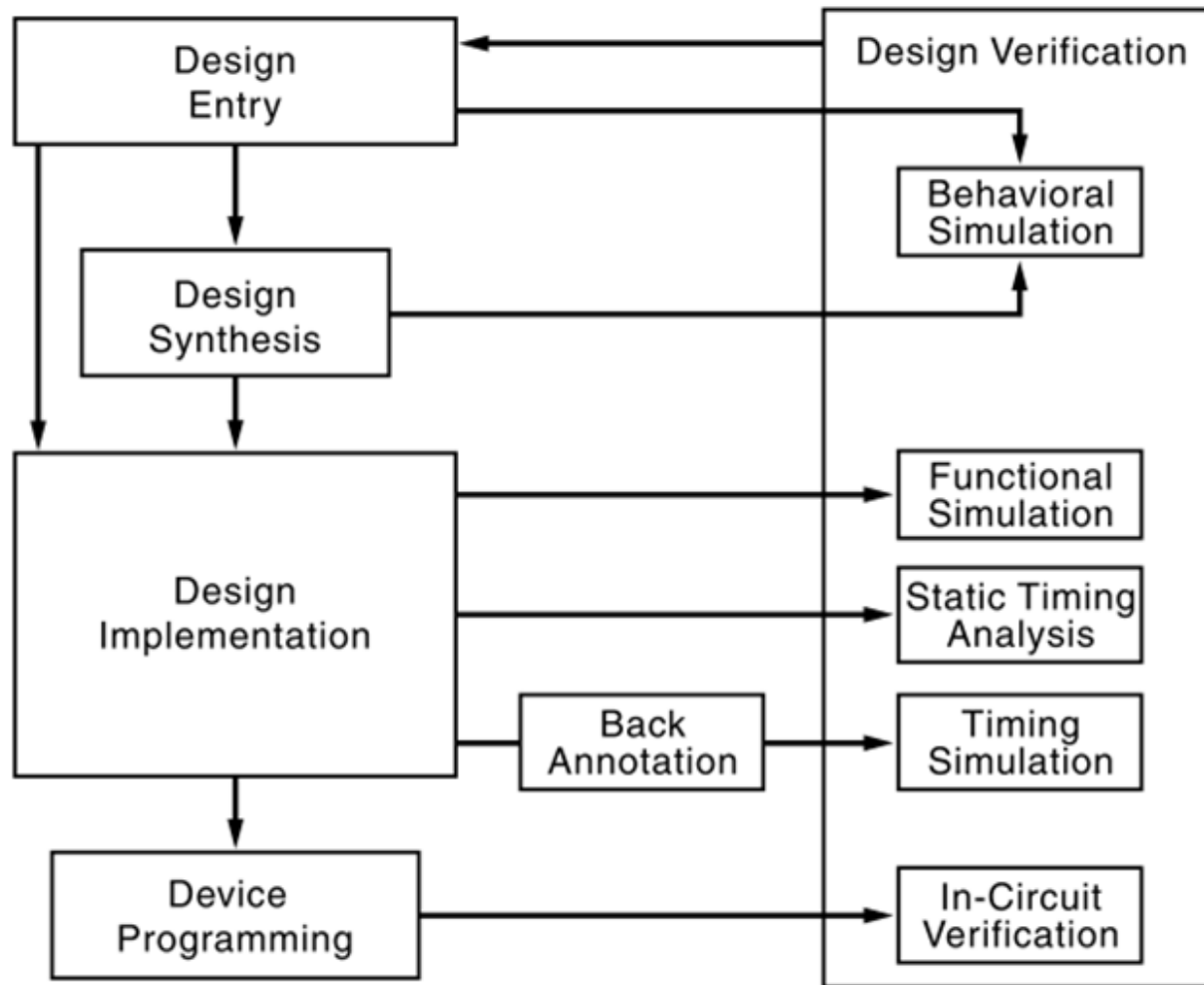


 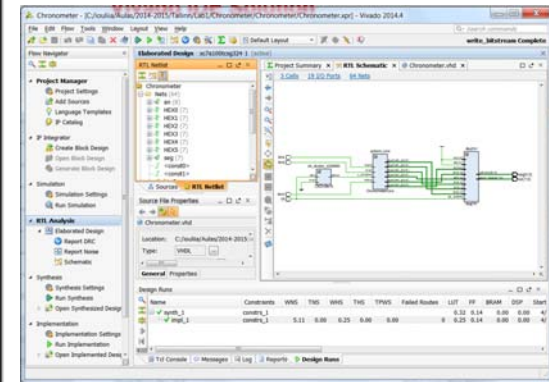- Design entry based on:
  - VHDL
  - IP Catalog






# Getting started page

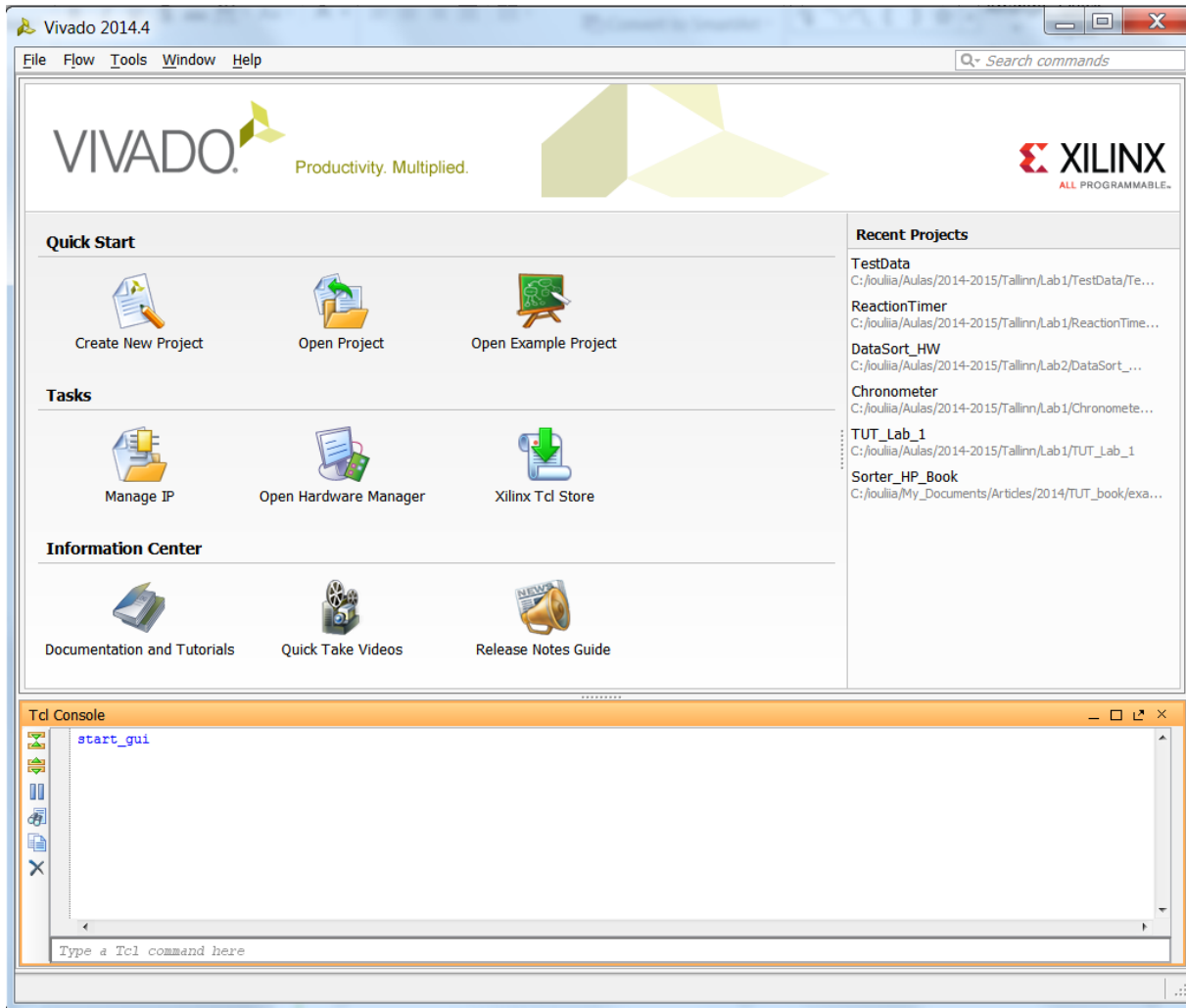


- Quick Start
  - Create new projects
  - Access to previous and example projects
- Tasks
  - IP management
  - Hardware Manager
  - Tcl store
- Information Center
  - Documents
  - Tutorials
  - Videos
- Tcl console
  - Command line access

# Creating a new project

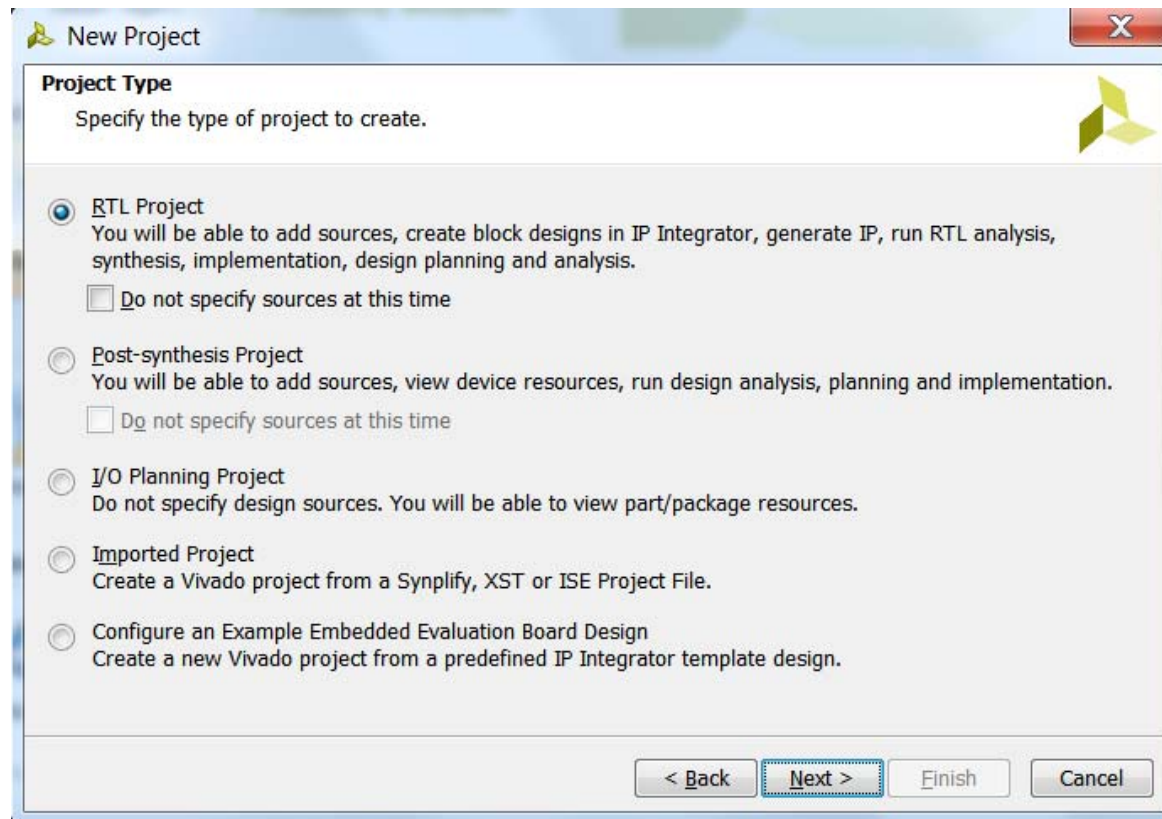

- Wizard guides through a creation of a new project
  - Define project name and location
  - Add source files
  - Specify target and simulator language
  - Add IPs
  - Add constraints
  - Select target device (**xc7a100tcsg324-1**)
- Different types of projects
  - RTL project
  - Import an existing project from ISE

# Flow Navigator

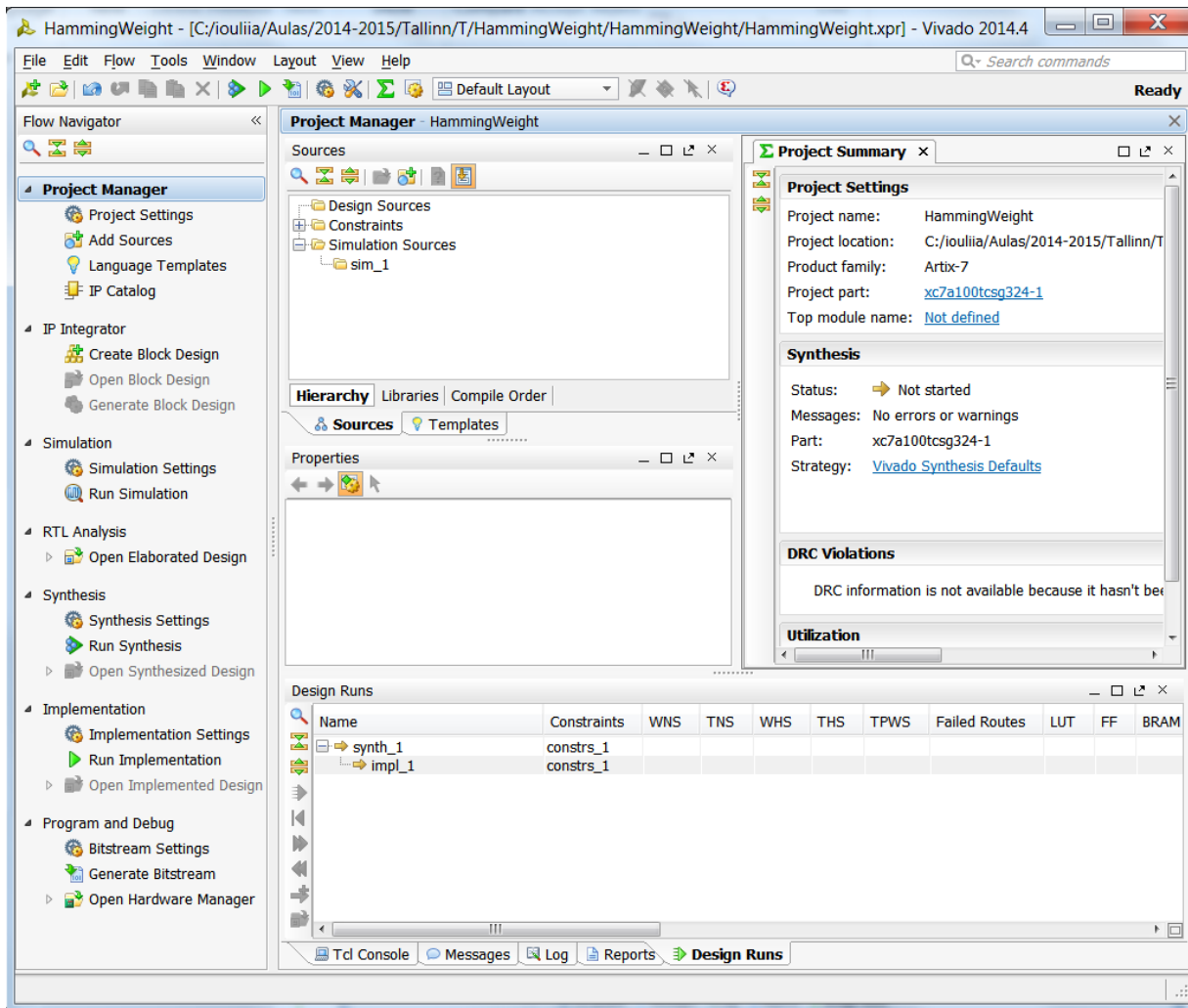

- Permits to manage project settings, add sources, customize IPs, launch simulation, execute RTL analysis, synthesis, implementation and device programming and debugging.
- Gives access to device utilization and timing summary

# A complete example

- Calculate the Hamming weight of a 16-bit vector using a sequential circuit
- The input vector is defined with Nexys-4 board switches
- The result should be displayed on LEDs
- Use the following components available:
  - Generic shift register (ShiftRegN.vhd)
  - Generic adder (AdderN.vhd)
  - Generic register (RegN.vhd)

# Adding design source files

**Project Manager - HammingWe**

Sources

- Design Sources
- Constraints
- Simulation Sources
- sim\_1

**Add Sources**

This guides you through the process of adding and creating sources for your project

- Add or create constraints
- Add or create design sources
- Add or create simulation sources
- Add or create DSP sources
- Add existing block design sources
- Add existing IP

**Add Sources**  
Specify and/or create source files to add to the project.

**Add Sources**

**Add or Create Design Sources**

Specify HDL and netlist files, or directories containing HDL and netlist files, to add to your project. Create a new source file on disk and add it to your project.

Index	Name	Library	Location
1	AdderN.vhd	xil_defaultlib	C:/ioulia/Aulas/2014-2015/Tallinn/T/HammingWeight/HammingWeight/HammingWe...
2	RegN.vhd	xil_defaultlib	C:/ioulia/Aulas/2014-2015/Tallinn/T/HammingWeight/HammingWeight/HammingWe...
3	ShiftRegN.vhd	xil_defaultlib	C:/ioulia/Aulas/2014-2015/Tallinn/T/HammingWeight/HammingWeight/HammingWe...

Scan and add RTL include files into project

Copy sources into project

Add sources from subdirectories

**Project Manager - HammingWeight**


Sources

- Design Sources (3)
  - AdderN - RTL (AdderN.vhd)
  - RegN - RTL (RegN.vhd)
  - ShiftRegN - RTL (ShiftRegN.vhd)
- Constraints
- Simulation Sources (3)
  - sim\_1 (3)
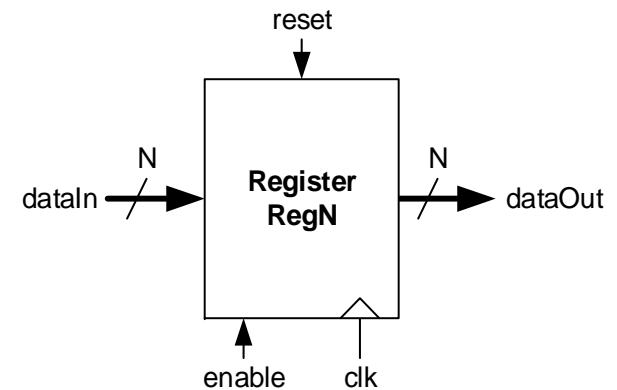
# Generic register (RegN.vhd)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity RegN is
    generic(N      : positive := 8);
    port(reset     : in  std_logic;
          clk      : in  std_logic;
          enable   : in  std_logic;
          dataIn   : in  std_logic_vector(N-1 downto 0);
          dataOut  : out std_logic_vector(N-1 downto 0));
end RegN;

architecture RTL of RegN is
begin
    process(clk)
    begin
        process(clk)
        begin
            if rising_edge(clk) then
                if reset = '1' then dataOut <= (others => '0');
                elsif en = '1' then dataOut <= dataIn;
                end if;
            end if;
        end process;
    end process;
end RTL;
```




Is reset synchronous or asynchronous?

# Generic adder (AdderN.vhd)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

entity AdderN is
  generic (N : positive := 4);
  port(A, B      : in std_logic_vector(N-1 downto 0);
       result   : out std_logic_vector(N-1 downto 0));
end AdderN;

 architecture RTL of AdderN is
begin
  result <= std_logic_vector(unsigned(A) + unsigned(B));
end RTL;
```



What is the difference between signed and unsigned additions?


# Generic shift register (ShiftRegN.vhd)

```
entity ShiftRegN is
  generic (N : positive := 4);
  port(clk      : in  std_logic;
        load    : in  std_logic;
        dataIn  : in  std_logic_vector(N-1 downto 0);
        serOut  : out std_logic);
end ShiftRegN;

architecture RTL of ShiftRegN is
  signal s_shiftReg : std_logic_vector(N-1 downto 0);
begin
  process(clk)
  begin
    if rising_edge(clk) then
      if load = '1' then      s_shiftReg <= dataIn;
      else                    s_shiftReg <= '0' & s_shiftReg(N-1 downto 1);
      end if;
    end if;
  end process;

  serOut <= s_shiftReg(0);

end RTL;
```

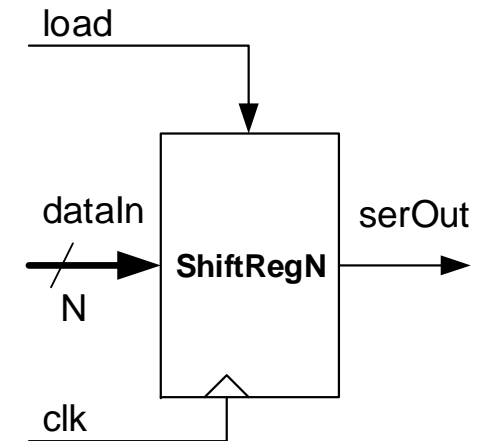

What is the direction of shift?



# Specifying constraints

Flow Navigator

Project Manager - HammingWe

Sources

- Design Sources
- Constraints
- Simulation Sources
- sim\_1

**Add Sources**

This guides you through the process of adding and creating sources for your project

- Add or create constraints
- Add or create design sources
- Add or create simulation sources
- Add or create DSP sources
- Add existing block design sources
- Add existing IP

**Add Sources**  
Specify and/or create source files to add to the project.


Add Constraint Files

Look in: HammingWeight

Name	Size	Item type	Date modified
HammingWeight.cache		File folder	28/04/2015 ...
HammingWeight.xpr	4.27 KB	Vivado Pr...	28/04/2015 ...
Nexys4_Master.xdc	37.8 KB	XDC File	04/09/2013 ...

- XDC file
  - Pin locations
  - Clock properties
  - Case-sensitive

# Nexys-4 XDC file

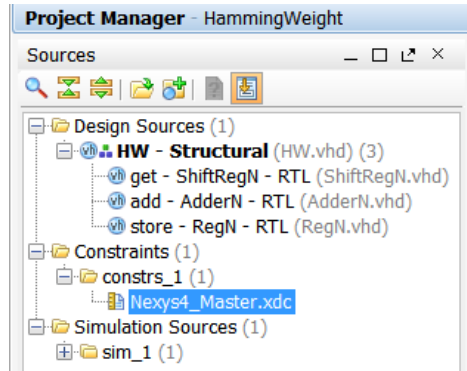

The Project Manager window shows the following sources and constraints:

- Design Sources (1)
  - HW - Structural (HW.vhd) (3)
    - get - ShiftRegN - RTL (ShiftRegN.vhd)
    - add - AdderN - RTL (AdderN.vhd)
    - store - RegN - RTL (RegN.vhd)
- Constraints (1)
  - constrs\_1 (1)
    - Nexys4\_Master.xdc
- Simulation Sources (1)
  - sim\_1 (1)

The block diagram shows a block labeled "HW" with the following connections:

- Input: `sw(15..0)` (16 bits)
- Input: `clk`
- Output: `led(4..0)` (5 bits)
- Input: `btnC`

```
1 ## This file is a general .xdc for the Nexys4 rev B board
2 ## To use it in a project:
3 ## - uncomment the lines corresponding to used pins
4 ## - rename the used ports (in each line, after get_ports) according to the top level
5
6 ## Clock signal
7 ##Bank = 35, Pin name = IO_L12P_T1_MRCC_35, Sch name = CLK100MHZ
8 set_property PACKAGE_PIN E3 [get_ports clk]
9 set_property IOSTANDARD LVCMOS33 [get_ports clk]
10 create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]
11
12 ## Switches
13 ##Bank = 34, Pin name = IO_L21P_T3_DQS_34, Sch name = SW0
14 set_property PACKAGE_PIN U9 [get_ports {sw[0]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {sw[0]}]
16 #Bank = 34, Pin name = IO_25_34, Sch name = SW1
17 set_property PACKAGE_PIN U8 [get_ports {sw[1]}]
18 set_property IOSTANDARD LVCMOS33 [get_ports {sw[1]}]
19 #Bank = 34, Pin name = IO_L23P_T3_34, Sch name = SW2
20 set_property PACKAGE_PIN R7 [get_ports {sw[2]}]
21 set_property IOSTANDARD LVCMOS33 [get_ports {sw[2]}]
22 #Bank = 34, Pin name = IO_L19P_T3_34, Sch name = SW3
23 set_property PACKAGE_PIN R6 [get_ports {sw[3]}]
24 set_property IOSTANDARD LVCMOS33 [get_ports {sw[3]}]
25 #Bank = 34, Pin name = IO_L19N_T3_VREF_34, Sch name = SW4
26 set_property PACKAGE_PIN R5 [get_ports {sw[4]}]
27 set_property IOSTANDARD LVCMOS33 [get_ports {sw[4]}]
28 #Bank = 34, Pin name = IO_L20P_T3_34, Sch name = SW5
29 set_property PACKAGE_PIN V7 [get_ports {sw[5]}]
30
31
32
33
34
35
36
37
38
39
40
41
42
43
44
45
46
47
48
49
50
51
52
53
54
55
56
57
58
59
60
61
62
63
64
65
66
67
68
69
70
71
72
73
74
75
76
77
78
79
80
81
82
83
84
85
86
87
88
89 ##Buttons
90 ##Bank = 15, Pin name = IO_L3P_T0_DQS_AD1P_15, Sch name = CPU_RESET
91 #set_property PACKAGE_PIN C12 [get_ports btnCpuReset]
92 #set_property IOSTANDARD LVCMOS33 [get_ports btnCpuReset]
93 #Bank = 15, Pin name = IO_L11N_T1_SRCC_15, Sch name = BTNC
94 set_property PACKAGE_PIN E16 [get_ports btnC]
95 set_property IOSTANDARD LVCMOS33 [get_ports btnC]
96 ##Bank = 15, Pin name = IO_L14P_T2_SRCC_15, Sch name = BTNU
97 #set_property PACKAGE_PIN F15 [get_ports btnU]
98 #set_property IOSTANDARD LVCMOS33 [get_ports btnU]
```

# Interconnecting the modules (HW.vhd)


```
entity HW is
  port( clk, btnC: in  std_logic;
        sw       : in std_logic_vector(15 downto 0);
        led      : out std_logic_vector(4 downto 0));
end HW;

architecture Structural of HW is
  signal s_en          : std_logic;
  constant s_value    : std_logic_vector(4 downto 0) := "00001";
  signal s_acc, s_add  : std_logic_vector(4 downto 0);
begin
  get: entity work.ShiftRegN(RTL)
    generic map(N => 16)
    port map (clk => clk, load => btnC, dataIn => sw, serOut => s_en);

  add: entity work.AdderN(RTL)
    generic map (N => 5)
    port map (A => s_value, B => s_acc, result => s_add);


  store: entity work.RegN(RTL)
    generic map (N => 5)
    port map (clk => clk, reset => btnC, en => s_en, dataIn => s_add, dataOut =>
s_acc);

  led <= s_acc;
end Structural;
```


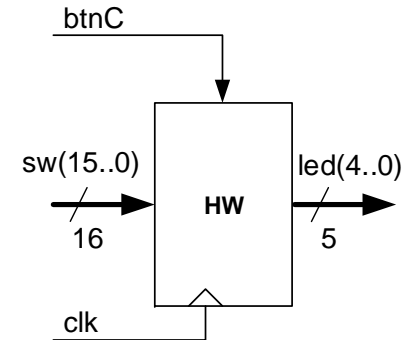

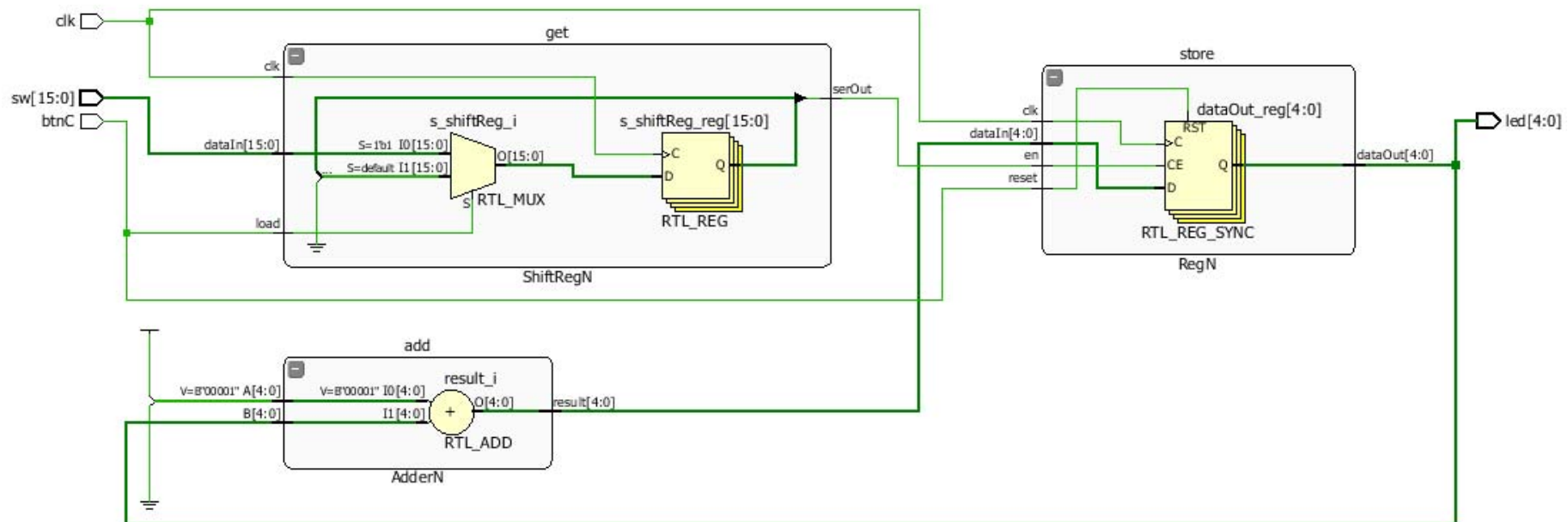
# Elaborated design

- Accessed through the Flow Navigator by selecting **Open Elaborated Design**
- Represents the design before synthesis
  - Instances of modules
  - Generic representation of hardware components
  - Interconnections





# Synthesis and the synthesized design

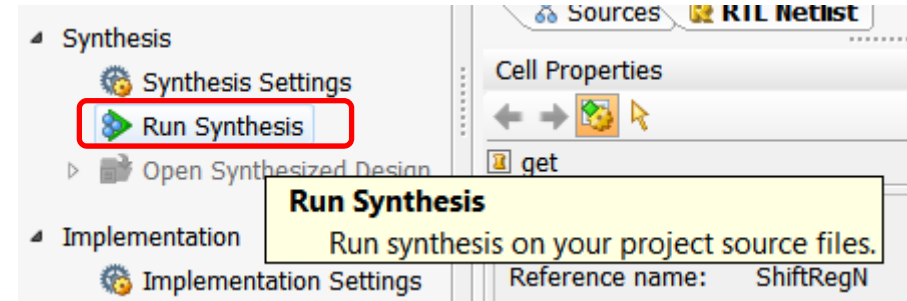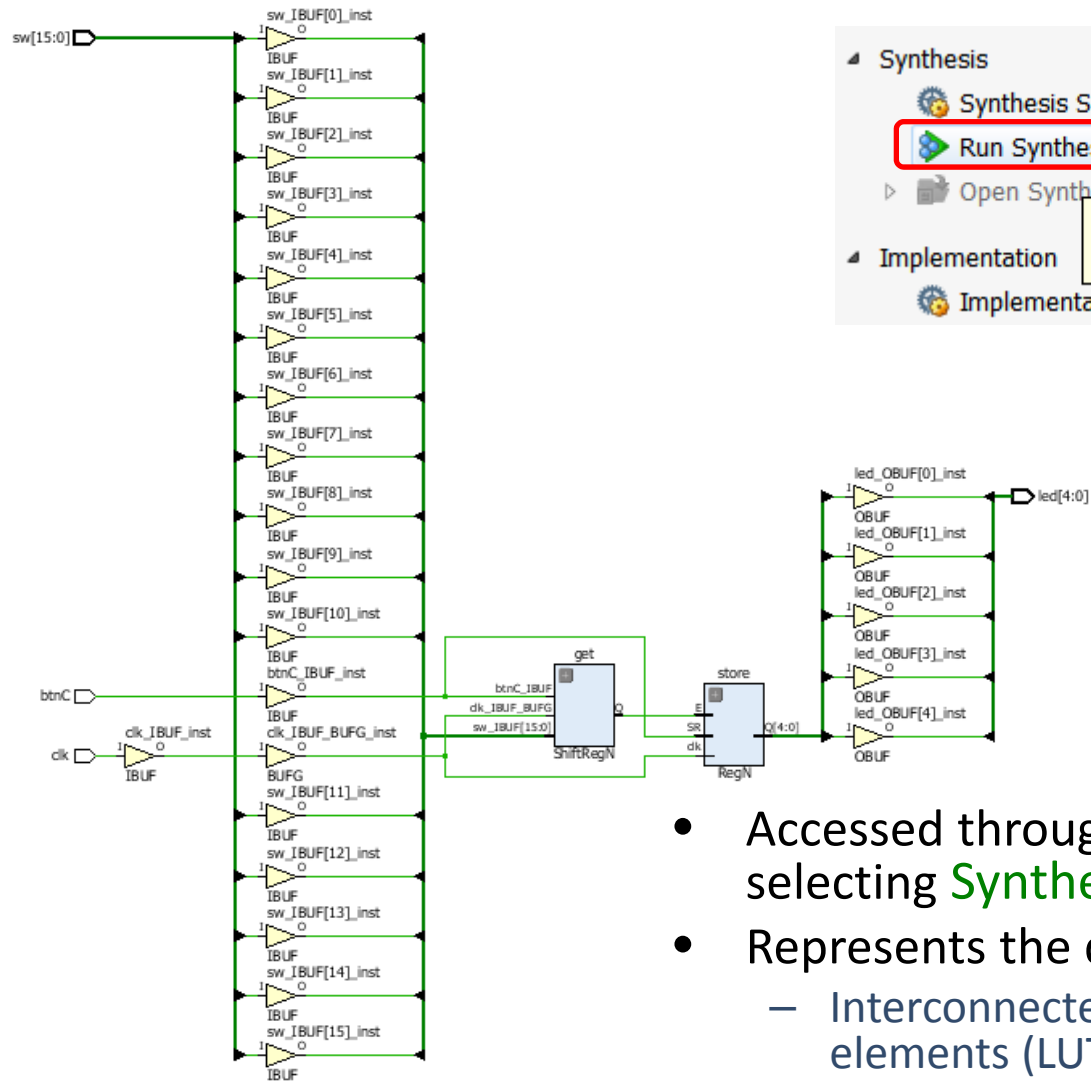

- Accessed through the Flow Navigator by selecting **Synthesized Design -> Schematic**
- Represents the design after synthesis
  - Interconnected netlist of modules and basic elements (LUTs, block RAMs, IBUFs, etc.)
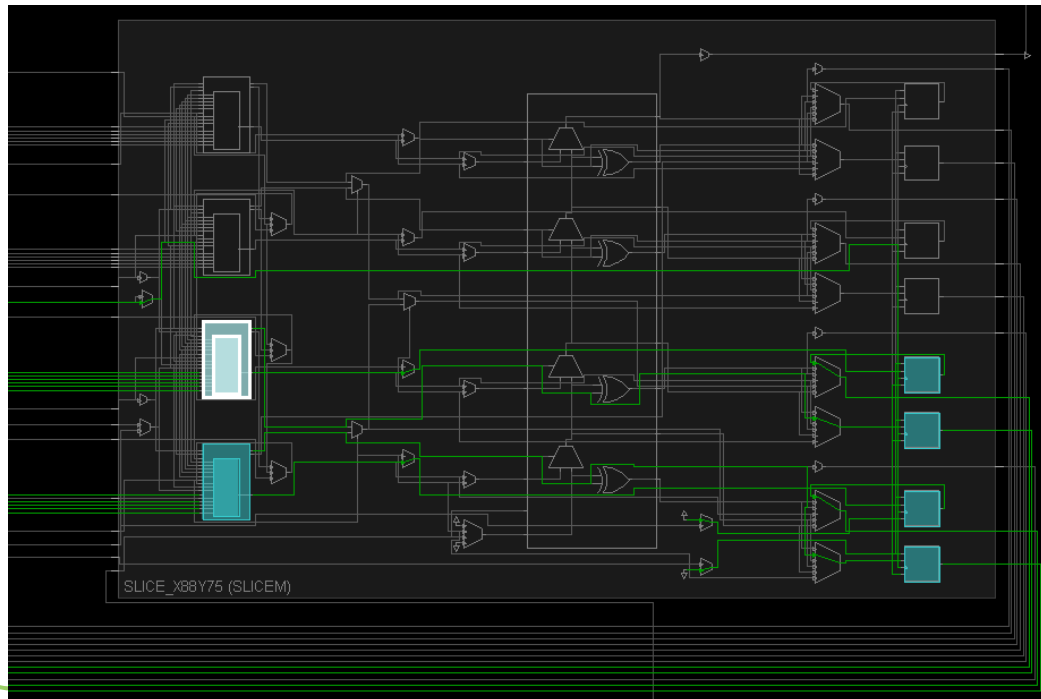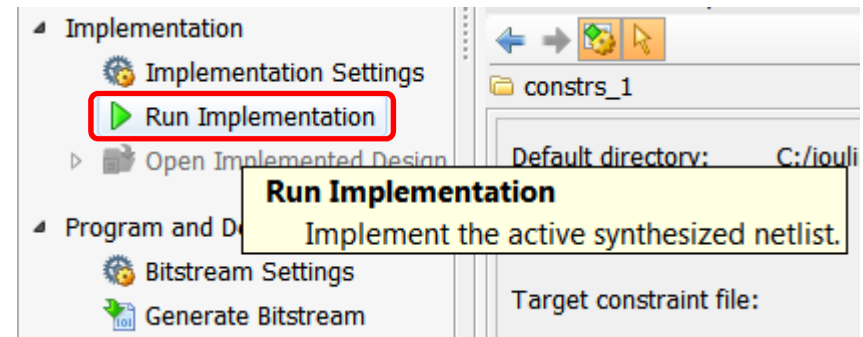
# Implementation and the implemented design

- Accessed after the implementation process by selecting **Open Implemented Design**
- Represents the design after the implementation
  - Structurally similar to the synthesized design
  - Cells have locations, and nets are mapped to specific routing resources



**Utilization - Post-Implementation**

Resource	Utilization	Available	Utilization...
FF	21	126800	0.02
LUT	11	63400	0.02
I/O	23	210	10.95
BUFG	1	32	3.12

Graph **Table**

Post-Synthesis **Post-Implementation**

# Reports

Name: get/s\_shiftReg[6]\_i\_1  
 Parent: get  
 Reference name: LUT3  
 Type: LUT  
 BEL: B6LUT Fixed  
 Site: SLICE\_X88Y75  
 Tile: CLBLM\_R\_X55Y75  
 Clock region: X1Y1  
 Number of cell pins: 4  
 Number of nets: 4

General Properties Power Nets Cell Pins Truth Table

Netlist Sources Properties

**Synthesis**

Status: ✔ Complete  
 Messages: No errors or warnings  
 Part: xc7a100tcsq324-1  
 Strategy: [Vivado Synthesis Defaults](#)

**DRC Violations**

Summary: ❗ 0 errors  
⚠ 0 critical warnings  
⚠ 1 warning  
ℹ 0 advisories

**Utilization - Post-Implementation**

Graph Table

Post-Synthesis **Post-Implementation**

**Implementation**

Status: ✔ Complete  
 Messages: ⚠ 1 warning  
 Part: xc7a100tcsq324-1  
 Strategy: [Vivado Implementation Defaults](#)  
 Incremental compile: [None](#)  
 Summary Route Status

**Timing - Post-Implementation**

Worst Negative Slack (WNS): 8.219 ns  
 Total Negative Slack (TNS): 0 ns  
 Number of Failing Endpoints: 0  
 Total Number of Endpoints: 25  
[Implemented Timing Report](#)

Setup Hold Pulse Width

Post-Synthesis **Post-Implementation**

**Power**

Total On-Chip Power: **0.098 W**  
 Junction Temperature: **25.4 °C**  
 Thermal Margin: 59.6 °C (12.9 W)  
 Effective θJA: 4.6 °C/W  
 Power supplied to off-chip devices: 0 W  
 Confidence level: [Low](#)

Summary On-Chip

Timing - Timing Summary - impl\_1

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): <span style="color: blue;">8.219 ns</span>	Worst Hold Slack (WHS): <span style="color: blue;">0.258 ns</span>	Worst Pulse Width Slack (WPWS): <span style="color: blue;">4.500 ns</span>
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 25	Total Number of Endpoints: 25	Total Number of Endpoints: 22

**All user specified timing constraints are met.**

Timing Summary - impl\_1

Universidade  
de Aveiro

# Errors and warnings


- Correct the XDC file

```
set_property CFGBVS VCCO [current_design]
set_property CONFIG_VOLTAGE 3.3 [current_design]
```


<b>Synthesis</b> ^	<b>Implementation</b> ^
Status: <span style="color: green;">✔</span> Complete Messages: No errors or warnings Part: xc7a100tcsg324-1 Strategy: <a href="#">Vivado Synthesis Defaults</a>	Status: <span style="color: green;">✔</span> Complete Messages: <span style="border: 2px solid red; padding: 2px;">No errors or warnings</span> Part: xc7a100tcsg324-1 Strategy: <a href="#">Vivado Implementation Defaults</a> Incremental compile: <a href="#">None</a> <b>Summary</b>   Route Status
<b>DRC Violations</b> ^	<b>Timing - Post-Implementation</b> ^
No DRC violations were found.	Worst Negative Slack (WNS): 8.219 ns Total Negative Slack (TNS): 0 ns Number of Failing Endpoints: 0 Total Number of Endpoints: 25 <a href="#">Implemented Timing Report</a> <b>Setup</b>   Hold   Pulse Width Post-Synthesis   <b>Post-Implementation</b>



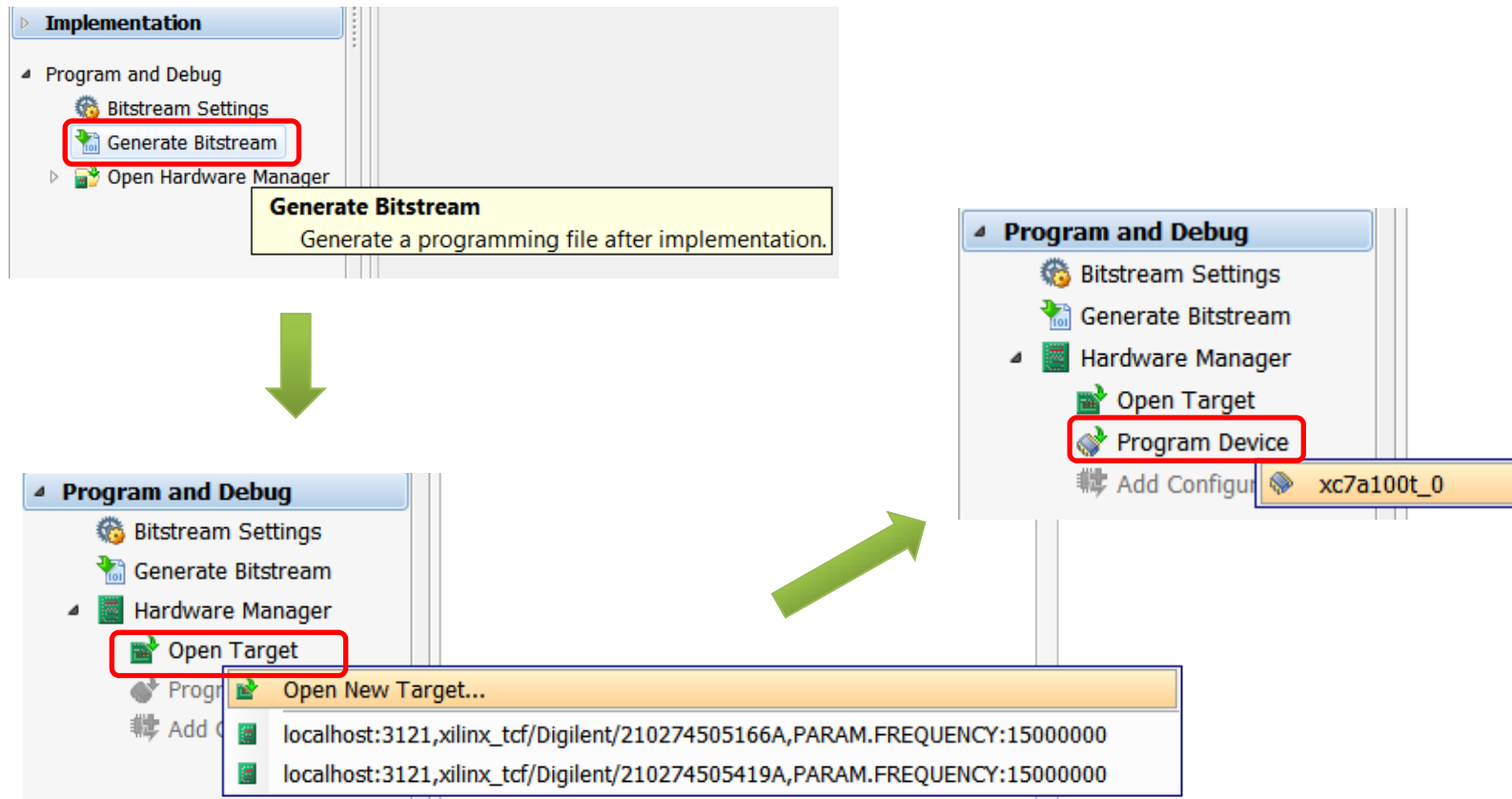
# Bitstream generation and device programming




# Design of test benches in VHDL

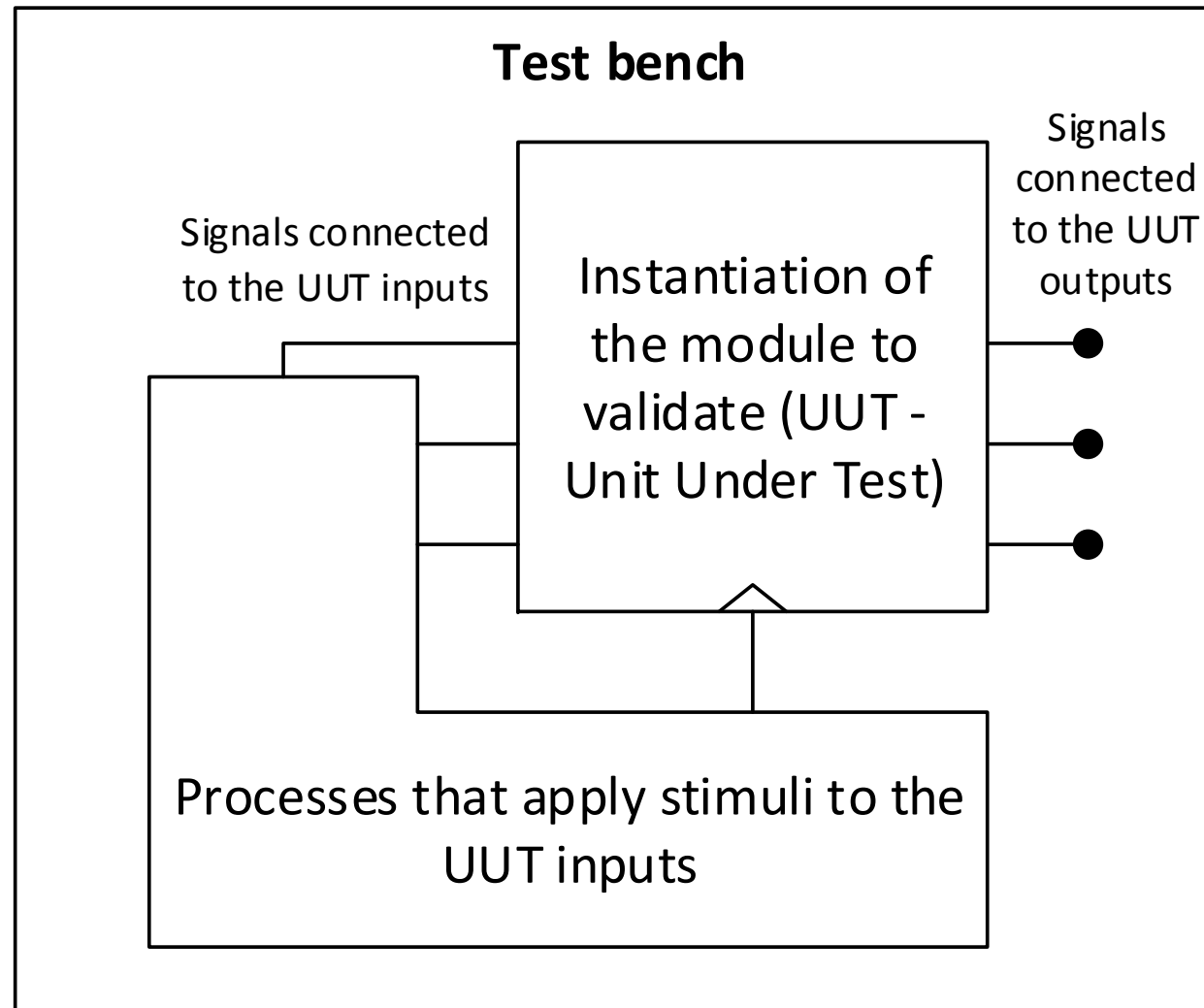

# Test benches for sequential UUTs

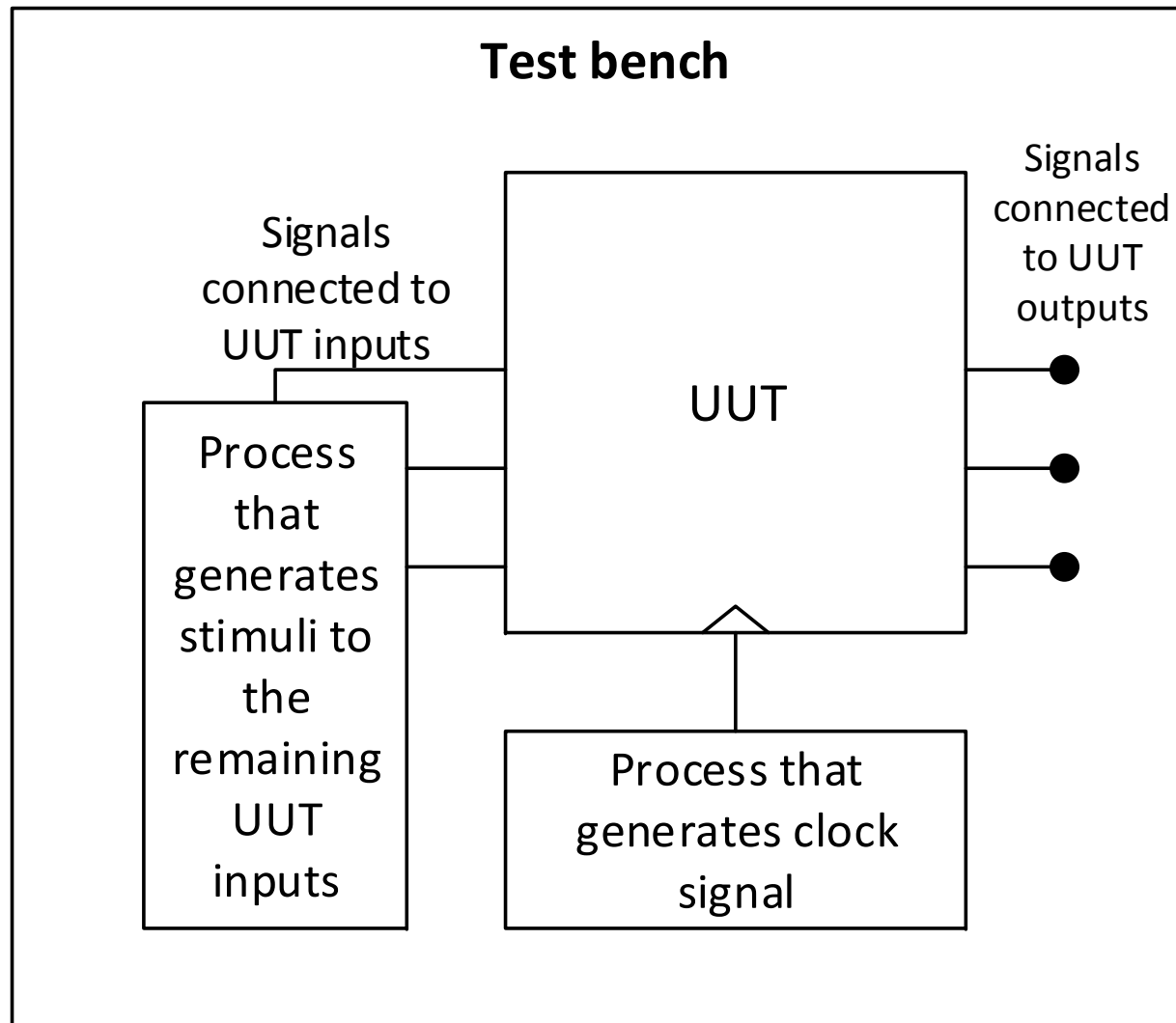



# Adding test bench files

 
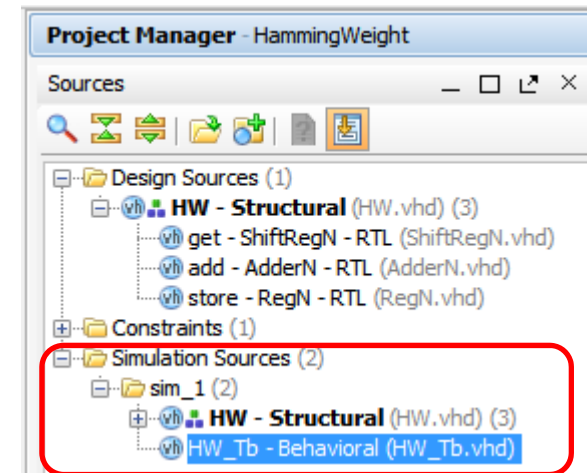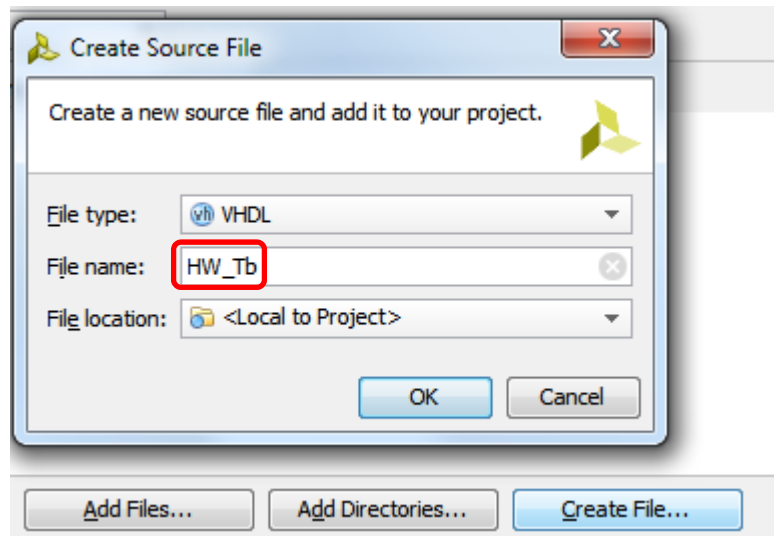
## Add Sources

This guides you through the process of adding and creating sources for your project


- Add or create constraints
- Add or create design sources
- Add or create simulation sources
- Add or create DSP sources
- Add existing block design sources
- Add existing IP


 
# Test bench for HW counter

```
-- Entity with no ports
entity HW_Tb is
end HW_Tb;

architecture Stimulus of HW_Tb is
  -- Signals to connect to UUT inputs
  signal s_reset, s_clk : std_logic;
  signal s_data          : std_logic_vector(15 downto 0);
  -- Signals to connect to UUT outputs
  signal s_result : std_logic_vector(4 downto 0);
begin
  -- Unit Under Test (UUT) instantiation
  uut : entity work.HW(Structural)
    port map (clk    => s_clk,
              btnC   => s_reset,
              sw     => s_data,
              led    => s_result);
  -- Process clock
  clock_proc : process
  begin
    s_clk <= '0'; wait for 10 ns;
    s_clk <= '1'; wait for 10 ns;
  end process;
```




```
--Process stim
stim_proc : process
begin
  s_reset <= '1';
  s_data  <= X"ABCD";
  wait for 20 ns;

  s_reset <= '0';
  wait for 400 ns;

  s_reset <= '1';
  s_data  <= X"8001";
  wait for 20 ns;



  s_reset <= '0';
  wait for 400 ns;
end process;
end Stimulus;
```

# Simulation in Vivado

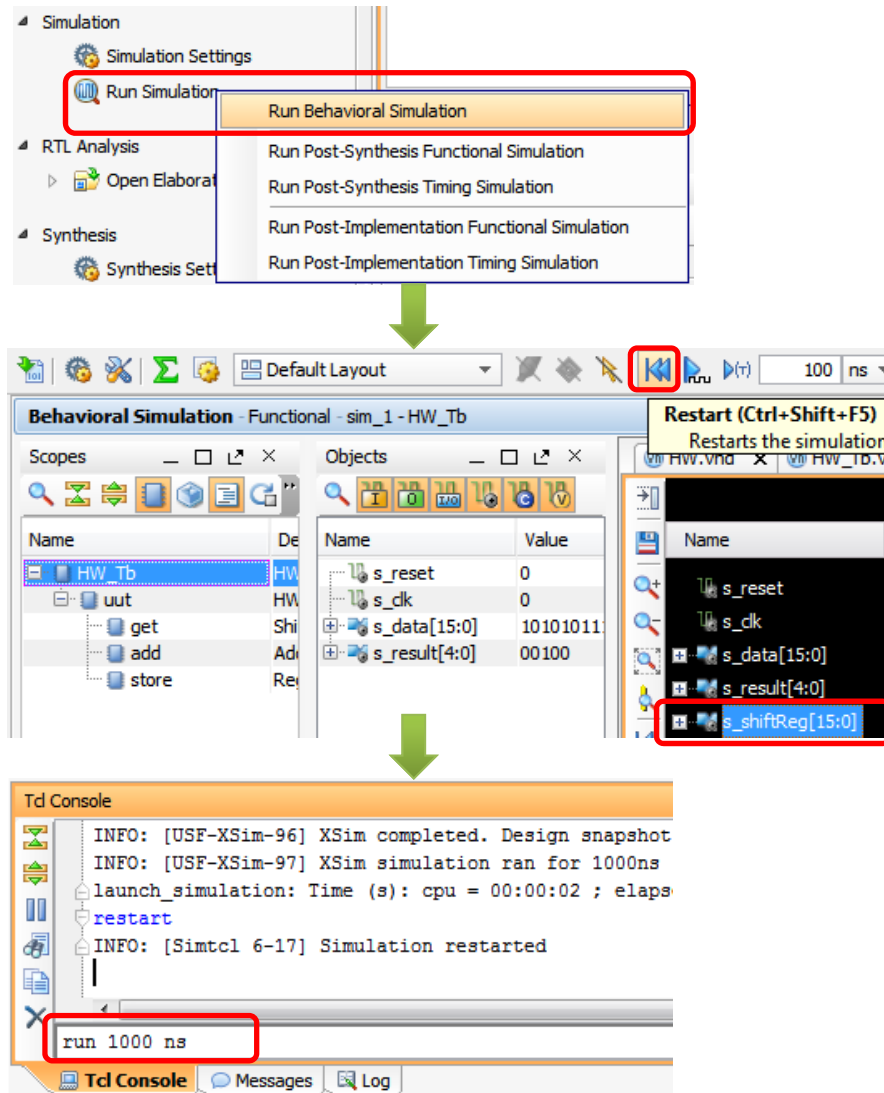

- Different simulation options are supported
- Possibility to add internal signals of UUT components
- Interaction with the simulator is done either through menus/buttons or via Tcl command line
- Standard waveform viewer options permit to change the scale, radix, etc.

# Simulation results

 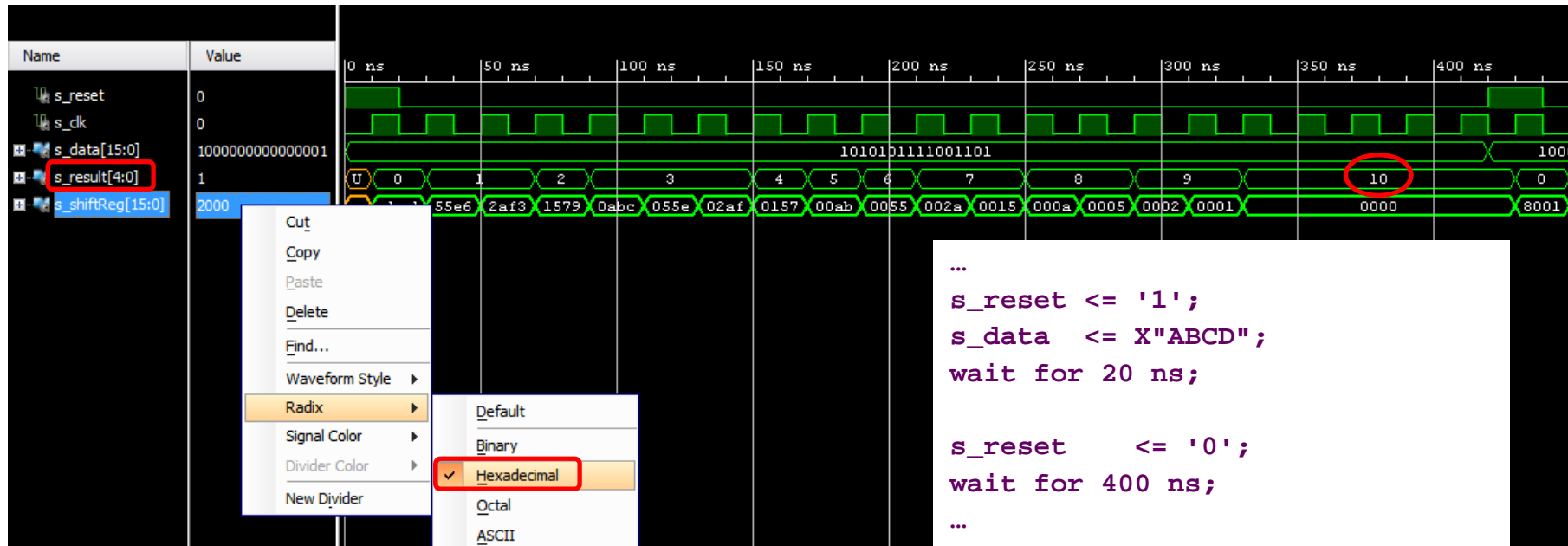

```

s_reset <= '1';
s_data <= X"8001";
wait for 20 ns;

```

```

s_reset <= '0';
wait for 400 ns;

```

# Some problems with simulation

Intended functionality	Incorrect specification	Comment
D flip-flop	<pre>process(clk) begin   if (clk = '1') then     dataOut &lt;= dataIn;   end if; end process;</pre>	Simulates correctly, <b>but</b> malfunctions in hardware!!!
D flip-flop with asynchronous reset	<pre>process(clk) begin   if (reset = '1') then     dataOut &lt;= '0';   elsif rising_edge(clk) then     dataOut &lt;= dataIn;   end if; end process;</pre>	Does not simulate correctly, <b>although</b> synthesizes and works correctly in hardware!!!

How to solve?





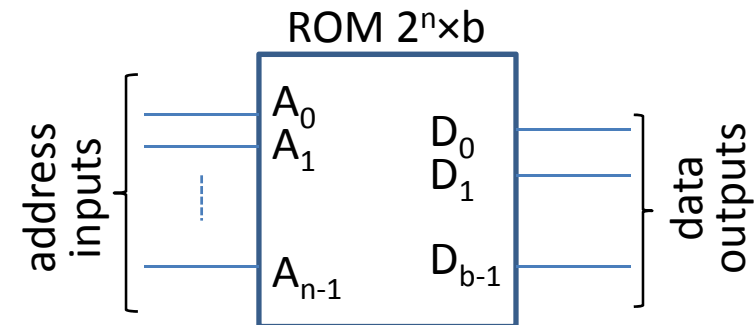
# Types of Memories


- *Read Only Memory* (**ROM**)

- Memory just for reading
- Any memory position can be accessed
- Useful for storing constants/non-changing data
  - Static tables
  - Messages, strings, etc.
- The content is defined at the time of manufacture or device programming



# Conceptual internal ROM structure

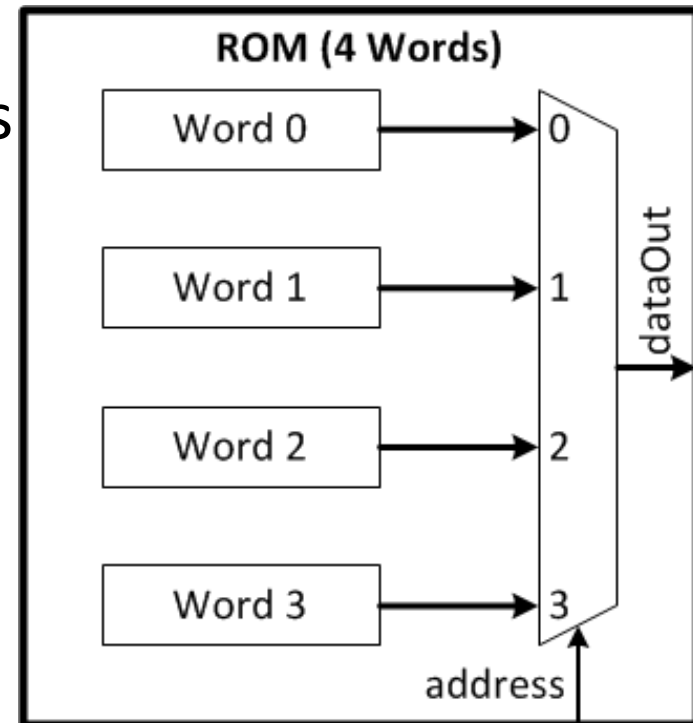- Example of a ROM for storing 4 words
- The size of *dataOut* is the same as the size of every memory word
- In this case, is reading synchronous or asynchronous?
- What is the size of the input *address*?
  - Usually power of 2
- What is the size of the input *address* for a ROM storing 1M words?




# Types of Memories

- *Random Access Memory* (**RAM**)
  - Memory for reading and writing
  - Any memory position can be accessed
  - Useful for storing data that can be changed during operation of the system
    - The content is written during system operation
  - Can have
    - 1 port (only one read or write operation in a given time)
    - Multi-port (various read or write operations in a given time)

# Conceptual internal RAM structure

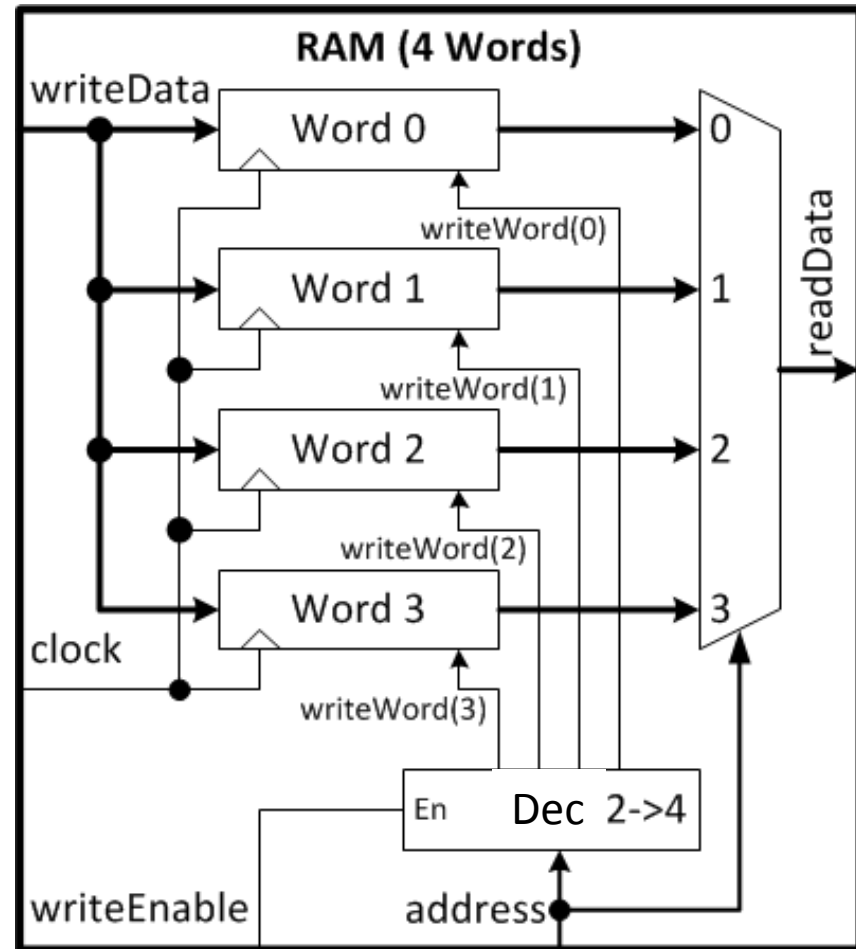- Example of a RAM for storing 4 words
- The size of data input *writeData* and data output *readData* is the same as the size of every memory word
- In this case
  - is reading synchronous or asynchronous?
  - is writing synchronous or asynchronous?



# Modeling a ROM

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.NUMERIC_STD.all;
```

**Subtype** defines a restricted set of values of its base type

```
entity ROM_8x4 is  
    port(address : in  std_logic_vector(2 downto 0);  
          dataOut : out std_logic_vector(3 downto 0));  
end ROM_8x4;
```

**Constant** allows to define constant values


```
architecture RTL of ROM_8x4 is  
    subtype TDataWord is std_logic_vector(3 downto 0);  
    type TROM is array (0 to 7) of TDataWord;  
    constant c_memory: TROM := ("0000", "0001", "0010", "0100",  
                                "1000", "1010", "1100", "1110");  
begin  
    dataOut <= c_memory(to_integer(unsigned(address)));  
end RTL;
```

**to\_integer** function converts (un)signed values to integers.
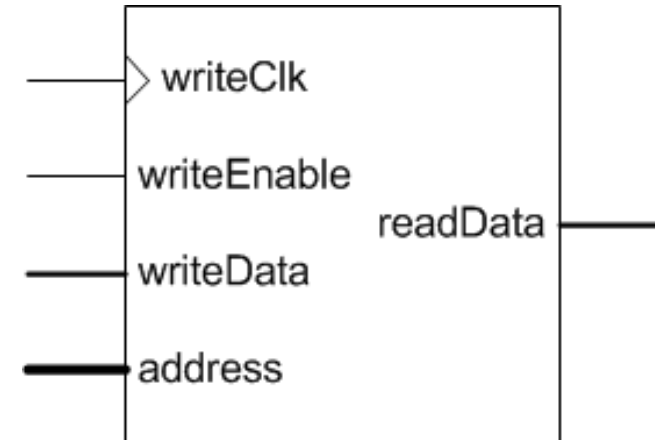
# Modeling a 32x8 bit RAM (1 port; asynchronous read) - entity

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

entity RAM_1_SW_AR is
    port(writeClk      : in  std_logic;
         writeEnable   : in  std_logic;
         writeData     : in  std_logic_vector(7 downto 0);
         address       : in  std_logic_vector(4 downto 0);
         readData      : out std_logic_vector(7 downto 0));
end RAM_1_SW_AR;
```



# Modeling a 32x8 bit RAM

## (1 port; asynchronous read) - architecture

architecture RTL of RAM\_1\_SW\_AR is

```
constant NUM_WORDS : integer := 32;  
subtype TDataWord is std_logic_vector(7 downto 0);  
type TMemory is array (0 to NUM_WORDS-1) of TDataWord;  
signal s_memory : TMemory;
```

begin

```
process(writeClk)
```

```
begin
```

```
    if (rising_edge(writeClk)) then
```

```
        if (writeEnable = '1') then
```

```
            s_memory(to_integer(unsigned(address))) <= writeData;
```

```
        end if;
```

```
    end if;
```

```
end process;
```


```
readData <= s_memory(to_integer(unsigned(address)));
```

```
end RTL;
```
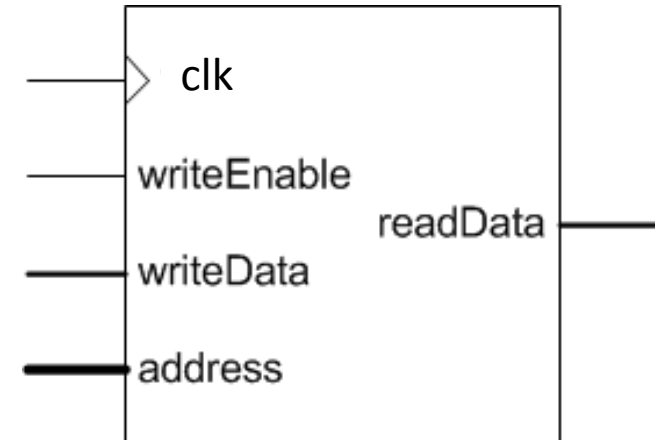
# Modeling a parameterizable RAM (1 port; synchronous read) - entity

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

entity RAM_2_SW_AR is
    generic(addrBusSize : integer := 4;
           dataBusSize : integer := 8);
    port(clk           : in  std_logic;
         writeEnable   : in  std_logic;
         address       : in  std_logic_vector((addrBusSize - 1) downto 0);
         writeData     : in  std_logic_vector((dataBusSize - 1) downto 0);
         readData      : out std_logic_vector((dataBusSize - 1) downto 0));
end RAM_2_SW_AR;
```






# Modeling a parameterizable RAM (1 port; synchronous read) – arch.

```
architecture RTL of RAM_2_SW_AR is
    constant NUM_WORDS : integer := (2 ** addrBusSize);
    subtype TDataWord is std_logic_vector((dataBusSize - 1) downto 0);
    type TMemory is array (0 to NUM_WORDS-1) of TDataWord;
    signal s_memory : TMemory;

begin
    process(clk)
    begin
        if (rising_edge(clk)) then
            if (writeEnable = '1') then
                s_memory(to_integer(unsigned(address))) <= writeData;
            end if;
        end if;
    end process;

     read_proc : process(clk) --read-first mode
    begin
        if (rising_edge(clk)) then
            readData <= s_memory(to_integer(unsigned(address)));
        end if;
    end process;
end RTL;
```



**read-first:** old content is read  
before new content is loaded

How to instantiate a  
64Kx32 RAM?



# Initialization of memories from files


- ROM/RAM contents can be initialized during synthesis from a text file.
- Example of a test file “data.dat”:

```
00000001
00000010
00000011
00000100
00000101
00000110
00000111
00001000
00001001
00001010
00001011
00001100
00001101
00001110
00001111
11111000
```
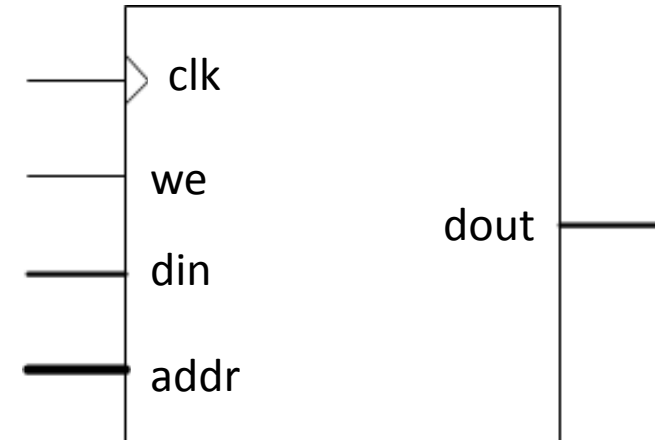
# Initializing a 16x8 bit RAM (1 port; synchronous read) - entity

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use std.textio.all;
use IEEE.NUMERIC_STD.ALL;

entity BRAM_ini is
    port (clk      : in std_logic;
          we       : in std_logic;
          addr     : in std_logic_vector(3 downto 0);
          din      : in std_logic_vector(7 downto 0);
          dout     : out std_logic_vector(7 downto 0));
end BRAM_ini;
```



The package `textio` declares the file type `text`, representing files of strings

# Initializing a 16x8 bit RAM (1 port; synchronous read) - function

```
architecture Behavioral of BRAM_ini is
    constant NUM_WORDS : integer := 16;
    subtype TDataWord is bit_vector(7 downto 0);
    type TMemory is array (0 to NUM_WORDS-1) of TDataWord;
```

```
    impure function InitRamFromFile (RamFileName : in string)
```

```
        return TMemory is
```

```
            FILE RamFile : text is in RamFileName;
```

```
            variable RamFileLine : line;
```

```
            variable RAM : TMemory;
```

```
            begin
```

```
                for I in TMemory'range loop
```

```
                    readline (RamFile, RamFileLine);
```

```
                    read (RamFileLine, RAM(I));
```

```
                end loop;
```

```
            return RAM;
```

```
        end function;
```

```
    signal RAM : TMemory := InitRamFromFile("Data.dat");
```

A function is **impure** if it refers to any variables or signals declared by its parents (any process, sub-program or architecture body in which the function declaration is nested)

# Working with files

- `readline` operation reads a complete line of text from an input file (*RamFile*).

```
readline (RamFile, RamFileLine);
```

- It creates a string object (*RamFileLine*) in the host computer's memory and returns a pointer to the string.
- We then use various versions of the read operation to extract values of different types from the string:

```
read (RamFileLine, RAM(I));
```

- Each version of read has at least two parameters: a pointer to the line of text from which to read (*RamFileLine*) and a variable in which to store the value (*RAM(I)*).
- For bit-vector values, the literal in the line should be a binary string without quotation marks or a base specifier (that is, just a string of '0' or '1' characters).

# Initializing a 16x8 bit RAM (1 port; synchronous read) – architecture

```
begin

process (clk) --write-first mode
  begin
    if clk'event and clk = '1' then
      if we = '1' then
        RAM(to_integer(unsigned(addr))) <= to_bitvector(din);
        dout <= din;
      else
        dout <= to_stdlogicvector(RAM(to_integer(unsigned(addr))));
      end if;
    end if;
  end process;

end Behavioral;
```

**write-first:** new content is immediately made available for reading (a.k.a. read-through)

A function `to_bitvector` converts a standard logic vector to a bit vector

A function `to_stdlogicvector` converts a bit vector to a standard logic vector

# Synthesis of memories

- Memory can be synthesized to either Distributed ROM/RAM (constructed from LUTs) or Block RAM (check the post-implementation resource utilization report).
- By default, the tool selects which RAM to infer, based upon heuristics that give the best results for most designs.
- Data is written **synchronously** into the RAM for both types.
- Reading is done **synchronously** for Block RAM and **asynchronously** for Distributed RAM.
- **ram\_style/rom\_style** attribute instructs the Vivado synthesis tool on how to infer memory:





```
signal RAM : TMemory := InitRamFromFile("Data.dat");  
attribute ram_style : string;  
attribute ram_style of RAM : signal is "block";  
attribute ram_style of RAM : signal is "distributed";
```

# FPGA memory resources

- The Artix-7™ FPGA xc7a100t-1csg324 contains 1,188 Kb of Distributed RAM and 4,860 Kb of Block RAM.
- Some of the key features of the Block RAM include:
  - Block RAMs are fundamentally 36 Kb in size; each block can also be used as two independent 18 Kb blocks. There are 135 36 Kb blocks.
  - Each block RAM has two completely independent ports that share nothing but the stored data (see Vivado Synthesis Guide for modeling dual-port RAMs).
  - Each memory access, read or write, is controlled by the clock.
  - Each port can be configured as  $32K \times 1$ ,  $16K \times 2$ ,  $8K \times 4$ ,  $4K \times 9$  (or 8),  $2K \times 18$  (or 16),  $1K \times 36$  (or 32), or  $512 \times 72$  (or 64).
  - The two ports can have different aspect ratios without any constraints.
  - During a write operation, the data output can reflect either the previously stored data (**read-first**), the newly written data (**write-first**), or can remain unchanged (**no-change**).



# Using IP Catalog

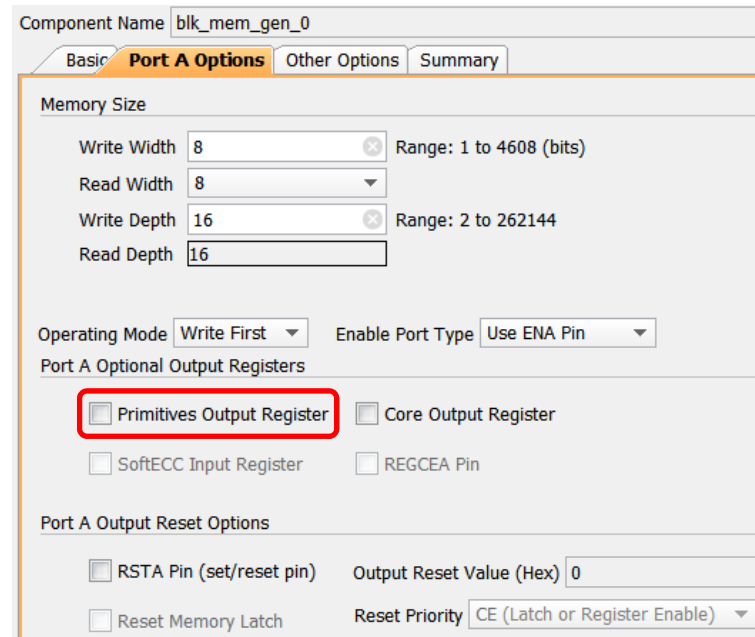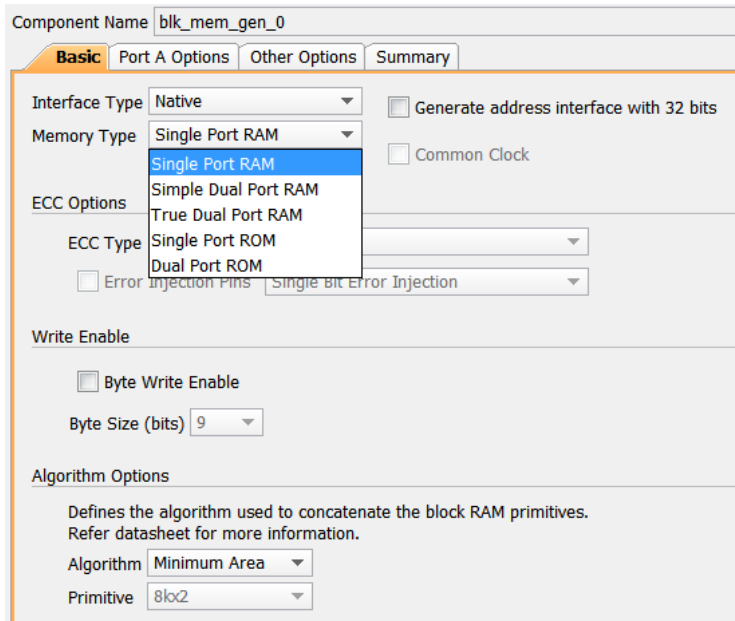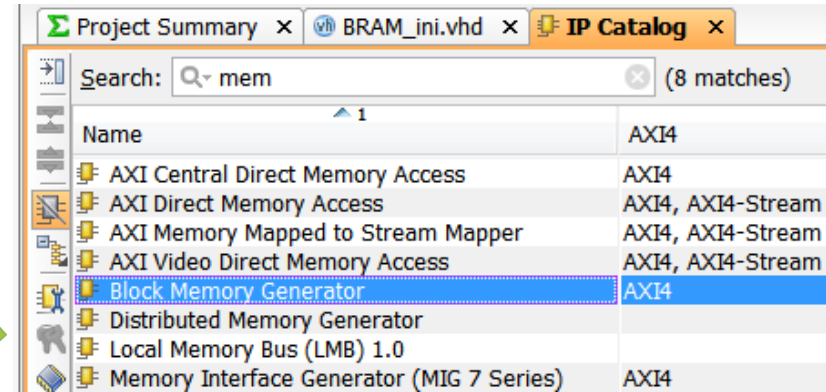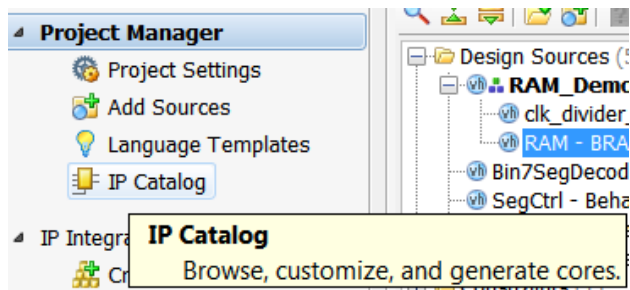

# Initialization from files

Basic Port A Options **Other Options** Summary

Pipeline Stages within Mux: 0 Mux Size: 1x1

Memory Initialization

Load Init File

Coe File:

Fill Remaining Memory Locations

Remaining Memory Locations (Hex):

Structural/UniSim Simulation Model Options

Defines the type of warnings and outputs are generated when a read-write or write-write collision occurs.

Collision Warnings:

Behavioral Simulation Model Options

Disable Collision Warnings  Disable Out of Range Warnings

Basic Port A Options Other Options **Summary**

Information

Memory Type: Single Port Memory

Block RAM resource(s) (18K BRAMs): 1

Block RAM resource(s) (36K BRAMs): 0

Total Port A Read Latency : 1 Clock Cycle(s)

Address Width A: 4

```
memory_initialization_radix = 16;
memory_initialization_vector = AB, BA, CD, DE, 99, 81, 71, 63,
                                A7, A6, 10, EC, 33, 71, 22, F4
```

# Instantiation of modules from the IP Catalog

The screenshot shows the Project Manager window with the Sources tree on the left. The tree is expanded to show the component `blk_mem_gen_0` under the `blk_mem_gen_0` block. The IP Catalog window on the right shows the VHDL code for the `blk_mem_gen_0` component, including the `ENTITY` and `PORT` declarations.

```
COMPONENT blk_mem_gen_0
PORT (
    clka : IN STD_LOGIC;
    ena  : IN STD_LOGIC;
    wea  : IN STD_LOGIC_VECTOR(0 DOWNTO 0);
    addra : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    dina : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
    douta : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
END COMPONENT;
```

```
BRAM: blk_mem_gen_0
    port map(clka => s_clk1Hz,
            ena  => std_logic('1'),
            wea  => s_wea,
            addra => sw(11 downto 8),
            dina  => sw(7 downto 0),
            douta => led);
```

# Useful modules for Lab 1


- Parameterizable clock divider
- Parameterizable debouncer
- 7-segment display control for Nexys-4

# Clock divider

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

entity ClkDividerN is
    generic(divFactor : positive);
    port(reset      : in  std_logic;
         clkIn     : in  std_logic;
         clkOut    : out std_logic);
end ClkDividerN;
```

```
architecture Behavioral of ClkDividerN is
    signal s_divCounter : natural;
begin
    process(reset, clkIn)
    begin
        process(reset, clkIn)
        begin
            if (reset = '1') then
                clkOut      <= '0';
                s_divCounter <= 0;
            elsif (rising_edge(clkIn)) then
                if (s_divCounter = divFactor - 1) then
                    clkOut      <= '0';
                    s_divCounter <= 0;
                else
                    if (s_divCounter = (divFactor / 2 - 1)) then
                        clkOut      <= '1';
                    end if;
                    s_divCounter <= s_divCounter + 1;
                end if;
            end if;
        end process;
    end process;
end Behavioral;
```

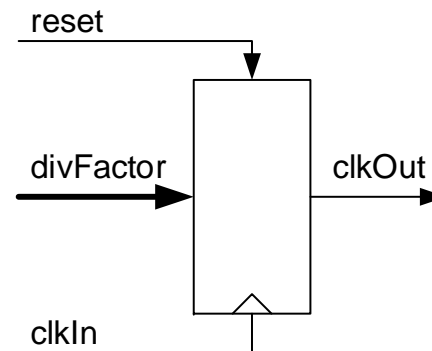

- The frequency division of a clock signal by integer factors, which are powers of 2, can be done by a binary counter
- The frequency division by arbitrary integer factors requires more elaborate hardware
- Example of a statically configurable frequency divider (*divFactor* is fixed at compile time upon instantiation with generic map)


# Simulation of the clock divider

Let  $f_{\text{clkIn}} = 50 \text{ MHz}$

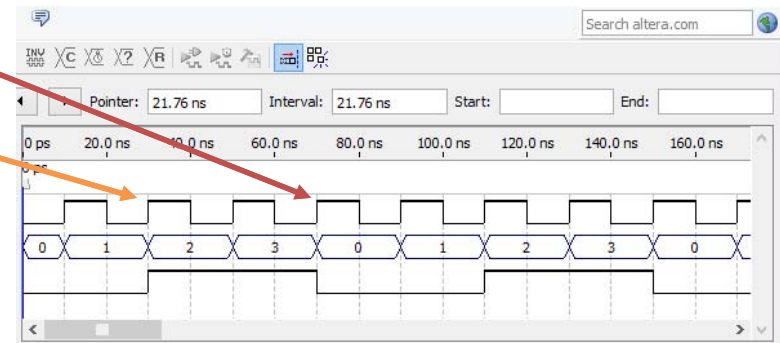**divFactor=4**


$f_{\text{clkOut}} ?$   
Duty cycle?

```
elseif (rising_edge(clkIn)) then
  if (s_divCounter = divFactor - 1) then
    clkOut      <= '0';
    s_divCounter <= 0;
  else
    if (s_divCounter = (divFactor / 2 - 1)) then
      clkOut      <= '1';
    end if;
    s_divCounter <= s_divCounter + 1;
  end if;
end if;
```




**divFactor=5**

$f_{\text{clkOut}} ?$   
Duty cycle?

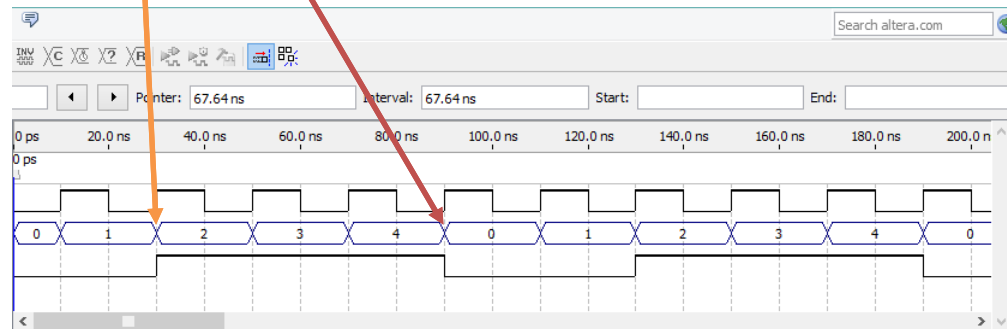


# Parameterizable debouncer

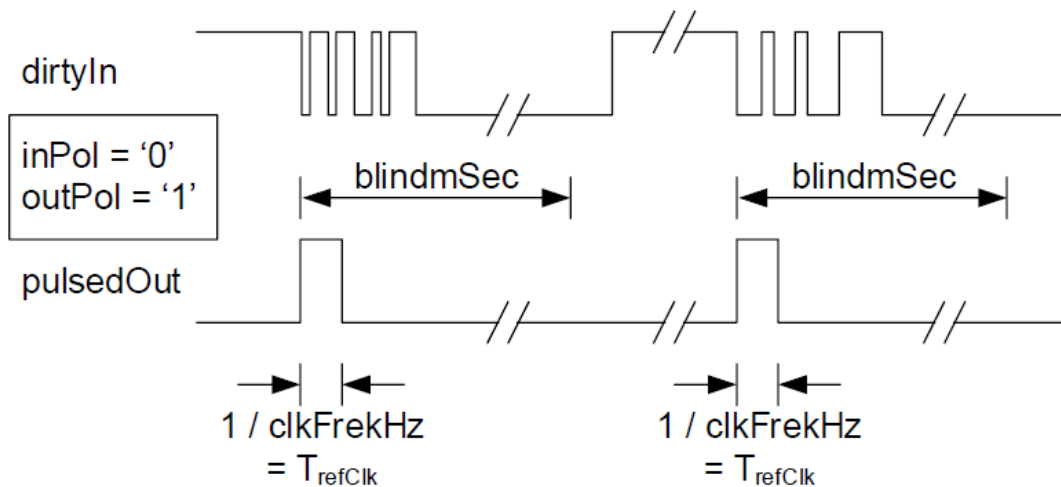

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

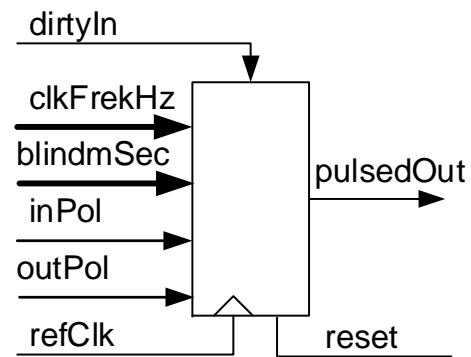entity DebounceUnit is
    generic (clkFreekHz    : positive;
            blindmSec     : positive;
            inPol          : std_logic;
            outPol         : std_logic);
    port ( reset          : in  std_logic;
          refClk         : in  std_logic;
          dirtyIn        : in  std_logic;
          pulsedOut      : out std_logic);
end DebounceUnit;
    
```



- Generic parameters:
  - **clkFreekHz** - frequency of the reference clock signal (in kHz)
  - **blindmSec** – blind time during which the circuit ignores input variations <1..100 ms>
  - **inPol** - input polarity ('0' for active low input; '1' for active high input)
  - **outPol** - output polarity ('0' for active low output; '1' for active high output)

# Parameterizable debouncer VHDL code

```

architecture Behavioral of DebounceUnit is
    signal s_dirtyIn, s_resetPulse, s_pulsedOut : std_logic;
    signal s_debounceCnt : natural;
begin
    sync_proc : process(refClk)
    begin
        if (rising_edge(refClk)) then
            s_dirtyIn <= dirtyIn;
        end if;
    end process;

    out_proc : process(reset, s_resetPulse, s_dirtyIn)
    begin
        if ((reset = '1') or (s_resetPulse = '1')) then
            s_pulsedOut <= not outPol;
        elsif ((s_dirtyIn'event) and s_dirtyIn = inPol) then
            s_pulsedOut <= outPol;
        end if;
    end process;



    pulsedOut <= s_pulsedOut;

```

```


timer_proc : process(reset, refClk)
begin
    if (reset = '1') then
        s_debounceCnt <= 0;
        s_resetPulse <= '0';
    elsif (rising_edge(refClk)) then
        if (s_debounceCnt /= 0) then
            s_debounceCnt <= s_debounceCnt - 1;
            s_resetPulse <= '1';
        elsif (s_pulsedOut = outPol) then
            s_debounceCnt <= blindmSec * clkFrekHHz;
            s_resetPulse <= '1';
        else
            s_resetPulse <= '0';
        end if;
    end if;
end process;
end Behavioral;

```

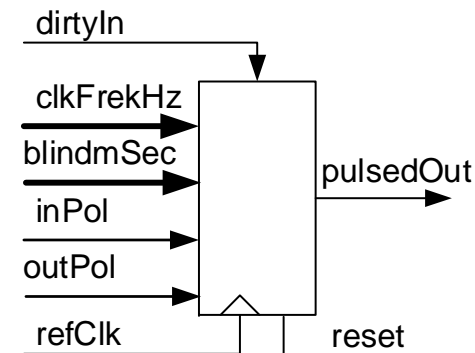 




# 7-segment display control for Nexys-4

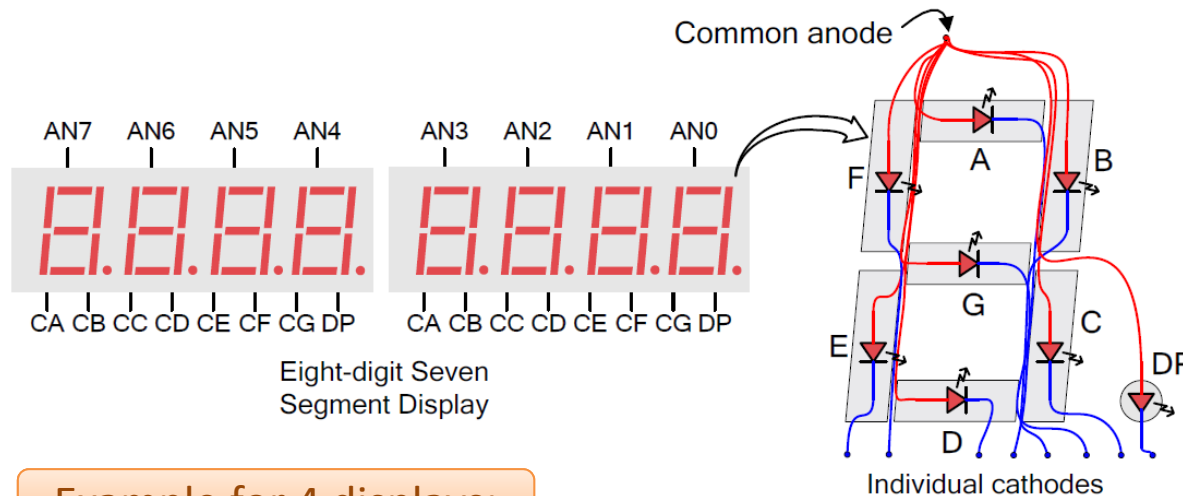

## Example for 4 displays:

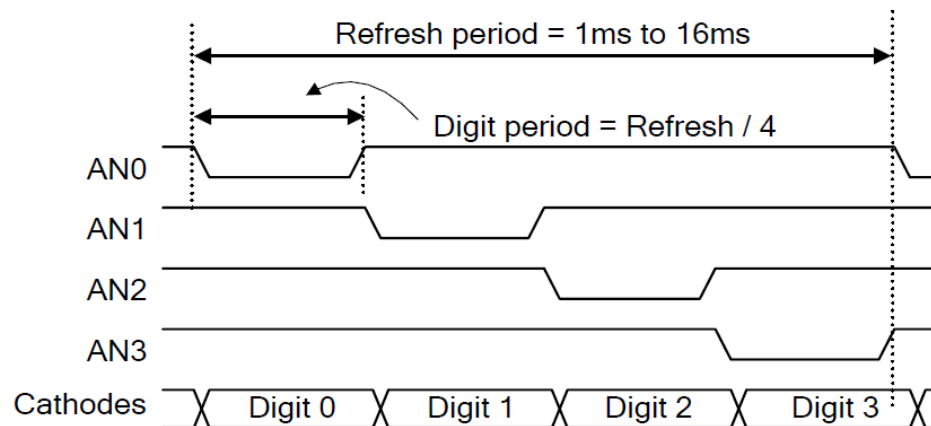

- The anodes of the seven LEDs forming each 7-segment display digit are tied together into one “common anode” circuit node.
- The LED cathodes remain separate. The cathodes of similar segments on all the displays are connected into seven circuit nodes.
- The common anode signals are available as eight “digit enable” input signals to the 8-digit display.
- The cathode signals are common to all digits but they can only illuminate the segments of the digit whose corresponding anode signal is asserted.
- To illuminate a segment, both the **anode** and the **cathode** are driven **low**.


# VHDL code of 7-segment display control for Nexys-4

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity SegCtrl is
  port ( clk_100MHz      : in  std_logic;
         SA, SB, SC, SD,
         SE, SF, SG, SH  : in  std_logic_vector (6 downto 0);
         cathodes        : out std_logic_vector (6 downto 0);
         select_display  : out std_logic_vector (7 downto 0));
end SegCtrl;

architecture Behavioral of SegCtrl is
  signal div      : unsigned(16 downto 0);
  signal clk_seg  : std_logic;
  signal state    : unsigned (2 downto 0);
begin

   -- clock divider
  divider: process(clk_100MHz)
  begin
    if rising_edge(clk_100MHz) then
      div <= div + 1;
      clk_seg <= div(div'left);
    end if;
  end process divider;
```



- Displays must be updated with a refresh frequency 60 Hz ... 1 KHz => clock period  $t$
- We generate 8 times higher frequency 480 Hz ... 8 KHz and activate each display for  $1/8$  of  $t$
- Division of 100 MHz by  $2^{17}$  gives  $\sim 763$  Hz

# VHDL code of 7-segment display control for Nexys-4

```
-- FSM that updates info on 7-segment displays in 8 cycles:
```

```
state_update: process (clk_seg)
```

```
begin
```

```
    if rising_edge(clk_seg) then
```

```
        state <= state + 1;
```

```
    end if;
```

```
end process state_update;
```

```
display_update: process (state, SA, SB, SC, SD, SE, SF, SG, SH)
```

```
begin
```

```
    case state is
```

```
        when "000" => cathodes <= SA; select_display <= "01111111";
```

```
        when "001" => cathodes <= SB; select_display <= "10111111";
```

```
        when "010" => cathodes <= SC; select_display <= "11011111";
```

```
        when "011" => cathodes <= SD; select_display <= "11101111";
```

```
        when "100" => cathodes <= SE; select_display <= "11110111";
```

```
        when "101" => cathodes <= SF; select_display <= "11111011";
```

```
        when "110" => cathodes <= SG; select_display <= "11111101";
```

```
        when "111" => cathodes <= SH; select_display <= "11111110";
```


```
        when others => cathodes <= (others => '1');
```

```
            select_display <= (others => '1');
```

```
    end case;
```

```
end process display_update;
```

```
end Behavioral;
```

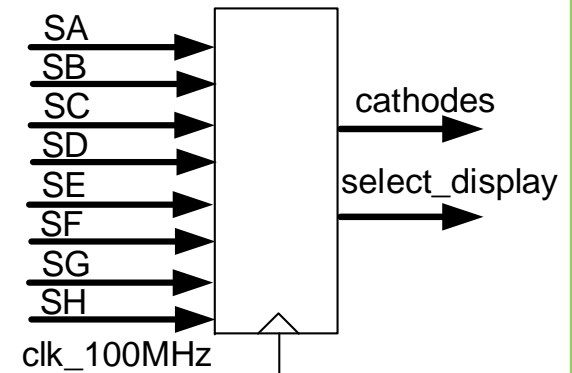

# Summary

- After completing this class and lab 1 you should be able to:
  - create and implement simple VHDL designs in Vivado Design Suite
  - configure the FPGA and interact with Nexys-4 prototyping board
  - develop VHDL test benches and simulate your designs in the integrated Vivado simulator
  - use appropriate coding styles to specify and initialize memories in VHDL
  - create and instantiate modules from the IP Catalog
  - employ in your designs modules such as:
    - parameterizable frequency divider
    - parameterizable debouncer
    - 7-segment display controller
- ... lab 1 is available at
  - [http://sweet.ua.pt/iouliia/Courses/PDP\\_TUT/index.html](http://sweet.ua.pt/iouliia/Courses/PDP_TUT/index.html)